

CSE260


Assignment 04

This assignment must be hand-written. Show ALL steps in ALL questions.
YOU NEED TO SUBMIT GRADED QUESTIONS ONLY.

GRADED QUESTIONS (1)

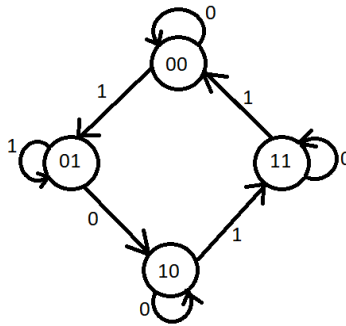Question 1 (10 Marks):

Given the state diagram as follows, get the sequential circuit using SR flipflop. Show all necessary tables.



Once you get the circuit diagram, try to build the above state diagram from your circuit diagram. Show all necessary tables.

UNGRADED QUESTIONS (2,3,4,5,6,7,8,9)

Question 2:

Implement the following counter using T flip flop

CSE110 -> CSE111 -> CSE220 -> CSE221 -> CSE331 -> CSE221 -> CSE321 -> CSE110

Question 3:

Draw the state diagram for the given circuit.

Draw the block diagram for a 1024x16 RAM.

