

CSE260: Digital Logic Design

Assignment 3

Submission Link Section 01: [Here](#)

Submission Link Section 02: [Here](#)

For all the following: Make sure that your circuit is efficient, meaning you should use the lowest number of components. You may use external gates if required.

Lecture - 7:

- ✓ 1. Build an adder-subtractor (4 bits)
- ✓ 2. Draw the block diagram of a 12-bit parallel adder.
- ✓ 3. Build a 13-person voting system using full and parallel adders.
- ✓ 4. Consider A is a 4-bit number. Design $A - 3$ using a 4-bit parallel adder. Use external gates if required.
- ✓ 5. Consider A is a 4-bit number. Design $A + 3$ using a 4-bit parallel adder. Use external gates if required.
- ✓ 6. Consider two numbers: 7 and 5. You can only calculate addition and subtraction between those two numbers. Design a circuit that can perform the above calculations based upon the user's intention.
- ✓ 7. Design a full adder using two half adders. You must use three NAND gates and no OR gates.
Design a full adder using two half adders. You must use two NOR gates and no OR gates.

Lecture - 8:

8. Construct a circuit with necessary components that convert a 3-bit 1s complement number to its actual 3-bit binary form.

9. Construct a circuit with necessary components that convert a 3-bit 2s complement number to its actual 3-bit binary form.
- ✓ 10. Implement the following boolean function using a single 16:1 mux.
 $F(A,B,C,D) = \sum(0,1,2,7,8,10,11,13, 15)$. Use external gates if required.
- ✓ 11. Implement the following boolean function using a single 8:1 mux.
 $F(A,B,C,D) = \sum(0,1,2,7,8,10,11,13, 15)$. Use external gates if required.
- ✓ 12. Implement the following boolean function using a single 4:1 mux.
 $F(A,B,C,D) = \sum(0,1,2,7,8,10,11,13, 15)$. Use external gates if required.
- ✓ 13. Implement the following boolean function using both 4:1 and 2:1 mux in a single circuit.
 $F(A,B,C,D) = \sum(0,1,2,7,8,10,11,13, 15)$. Use external gates if required.
- ✓ 14. Implement the following boolean function using
a) 4x16 decoder(s) only ✓
b) 2x4 decoder(s) only
 $F(A,B,C,D,E) = \sum(0,1,2,7,8,10,11,13, 15,18,21,24,25)$. Use external gates if required.
- ✓ 15. Build a BCD to Excess-3 code converter using encoder(s) and decoder(s).
- ✓ 16. Build a BCD to Excess-5 code converter using encoder(s) and decoder(s).