

Problem 1

- Perform **branch current analysis** to determine the current absorbed by the 6 V source in the following circuit.
- Perform **mesh analysis** to determine the current absorbed by the 6 V source in the following circuit.



Applying KVL in mesh 1,

$$-10 + 2i_1 + 8(i_1 - i_2) = 0$$

$$\Rightarrow -10 + 2i_1 + 8i_1 - 8i_2 = 0$$

$$\Rightarrow \boxed{10i_1 - 8i_2 = 10} \quad \text{--- (i)}$$

Applying KVL in mesh 2,

$$8(i_2 - i_1) + 4i_2 - 6 = 0$$

$$\Rightarrow 8i_2 - 8i_1 + 4i_2 - 6 = 0$$

$$\Rightarrow \boxed{8i_1 - 12i_2 = -6} \quad \text{--- (ii)}$$

Solving (i) & (ii),


$$\boxed{i_1 = 3A}$$

$$\boxed{i_2 = 2.5A}$$

Current absorbed by 6V source is $(-2.5A)$

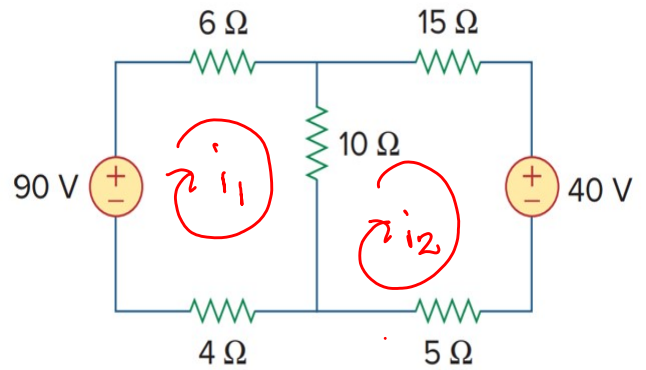Problem 2

- Calculate the current through the $10\ \Omega$ resistor using mesh analysis.



Applying KVL in mesh 1,

$$-90 + 6i_1 + 10(i_1 - i_2) + 4i_1 = 0$$

$$\Rightarrow -90 + 6i_1 + 10i_1 - 10i_2 + 4i_1 = 0$$

$$\Rightarrow \boxed{20i_1 - 10i_2 = 90} \quad \text{--- (1)}$$

Applying KVL in mesh 2,

$$10(i_2 - i_1) + 15i_2 + 40 + 5i_2 = 0$$

$$\Rightarrow 10i_2 - 10i_1 + 15i_2 + 40 + 5i_2 = 0$$

$$\Rightarrow \boxed{-10i_1 + 30i_2 = -40} \quad \text{--- (2)}$$

Solving (1) & (2),

$$\boxed{i_1 = 4.6\text{ A}}$$

$$\boxed{i_2 = 0.2\text{ A}}$$


Current through $10\ \Omega$ Resistor

$$i_1 - i_2 = 4.6 - 0.2$$

$$= \boxed{4.4\text{ A}}$$

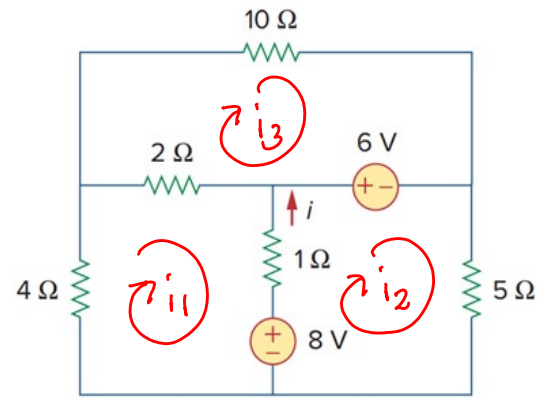Problem 3

- Calculate the current i using mesh analysis.



Applying KVL in mesh 1,

$$4i_1 + 2(i_1 - i_3) + 1(i_1 - i_2) + 8 = 0$$

$$\Rightarrow 4i_1 + 2i_1 - 2i_3 + i_1 - i_2 + 8 = 0$$

$$\Rightarrow \boxed{7i_1 - i_2 - 2i_3 = -8} \quad \text{--- (I)}$$

Applying KVL in mesh 2,

$$-8 + 1(i_2 - i_1) + 6 + 5i_2 = 0$$

$$\Rightarrow -8 + i_2 - i_1 + 6 + 5i_2 = 0$$

$$\Rightarrow \boxed{-i_1 + 6i_2 = 2} \quad \text{--- (II)}$$

Applying KVL in mesh 3,

$$10i_3 - 6V + 2(i_3 - i_1) = 0$$

$$\Rightarrow 10i_3 - 6V + 2i_3 - 2i_1 = 0$$


$$\Rightarrow \boxed{-2i_1 + 13i_3 = 6} \quad \text{--- (III)}$$

Solving (I), (II) & (III), $\boxed{i_1 = -1.03}$ $\boxed{i_2 = 0.16}$ $\boxed{i_3 = 0.30}$

$$i_o = (i_2 - i_1) \\ = 0.16 - (-1.03) = \boxed{1.19 \text{ A}}$$

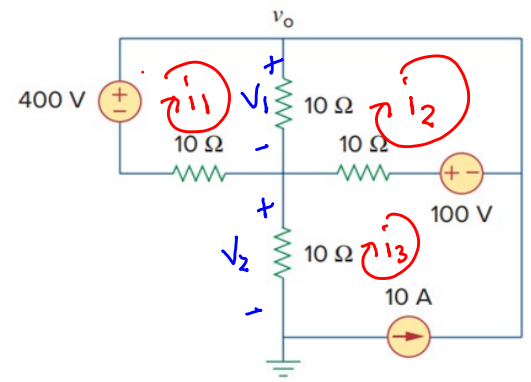Problem 4

- Apply mesh analysis to find v_o in the following circuit.



From the circuit,

$$i_3 = -10 \text{ A} \quad \text{--- (i)}$$

Applying KVL in the mesh 1,

$$-400 + 10(i_1 - i_2) + 10i_1 = 0$$

$$\Rightarrow -400 + 10i_1 - 10i_2 + 10i_1 = 0$$

$$\Rightarrow 20i_1 - 10i_2 = 400 \quad \text{--- (ii)}$$

Applying KVL in the mesh 2,

$$-100 + 10(i_2 - i_3) + 10(i_2 - i_1) = 0$$

$$\Rightarrow -100 + 10i_2 - 10i_3 + 10i_2 - 10i_1 = 0$$

applying $i_3 = -10 \text{ A}$,

$$-100 + 10i_2 - 10(-10) + 10i_2 - 10i_1 = 0$$

$$\Rightarrow -100 + 20i_2 - 10i_1 + 100 = 0$$

$$\Rightarrow -10i_1 + 20i_2 = 0 \quad \text{--- (iii)}$$

Solving (i) & (ii),

$$i_1 = 26.67 \text{ A}$$

$$i_2 = 13.33 \text{ A}$$

From the circuit,

$$V_o = V_1 + V_2$$

$$\begin{aligned} V_1 &= 10(i_1 - i_2) \\ &= 10 \times (26.67 - 13.33) \\ &= 133.4 \text{ V} \end{aligned}$$

$$\begin{aligned} V_2 &= 10 \times (-i_3) \\ &= 10 \times (-(-10)) \\ &= 100 \text{ V} \end{aligned}$$

$$\therefore V_o = 100 + 133.4$$

$$V_o = 233.4$$

Problem 5

- Find i_0 using mesh analysis. What is the voltage across the $0.5i_0$ source?

from circuit,

$$i_1 = 0.5i_0$$

from mesh 2,

$$i_2 = -i_0 \Rightarrow i_0 = -i_2$$

$$\therefore i_1 = 0.5(-i_2)$$

$$\Rightarrow i_1 + 0.5i_2 = 0 \quad \text{--- (I)}$$

Applying KVL in mesh 2,

$$1i_2 + 4(i_2 - i_1) + 280 = 0$$

$$\Rightarrow i_2 + 4i_2 - 4i_1 + 280 = 0$$

$$\Rightarrow 4i_1 - 5i_2 = 280 \quad \text{--- (II)}$$


Applying KVL in mesh 3,

$$-280 + 8(i_3 - i_1) + 2i_3 = 0$$

$$\Rightarrow -280 + 8i_3 - 8i_1 + 2i_3 = 0$$

$$\Rightarrow 8i_1 - 10i_3 = -280 \quad \text{--- (III)}$$

Solving (I), (II) & (III),

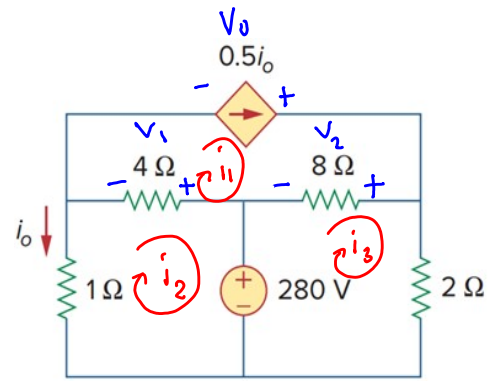

$$i_1 = 20A$$

$$i_2 = -40A$$

$$i_3 = 44A$$

Net voltage across 2Ω source is V_0 &

$$V_0 = V_1 + V_2$$


$$\begin{aligned} V_1 &= (i_1 - i_2) \times 4 \\ &= (20 - (-40)) \times 4 \\ &= 60 \times 4 = 240V \end{aligned}$$

$$\begin{aligned} V_2 &= (i_1 - i_3) \times 8 \\ &= (20 - 44) \times 8 \\ &= -192V \end{aligned}$$

$$\begin{aligned} \therefore V_0 &= V_1 - V_2 = 240 - 192 \\ &= 48V \end{aligned}$$

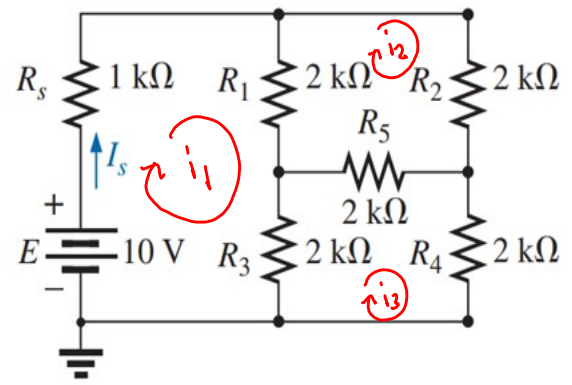Problem 6

- Determine the current through the source resistor R_s using mesh analysis.



Applying KVL in mesh 1,

$$-10 + 1 \cdot i_1 + 2(i_1 - i_2) + 2(i_1 - i_3) = 0$$

$$\Rightarrow -10 + i_1 + 2i_1 - 2i_2 + 2i_1 - 2i_3 = 0$$

$$\Rightarrow \boxed{5i_1 - 2i_2 - 2i_3 = 10} \quad \text{--- (I)}$$

Applying KVL in mesh 2,

$$2(i_2 - i_1) + 2i_2 + 2(i_2 - i_3) = 0$$

$$\Rightarrow 2i_2 - 2i_1 + 2i_2 + 2i_2 - 2i_3 = 0$$

$$\Rightarrow \boxed{-2i_1 + 6i_2 - 2i_3 = 0} \quad \text{--- (II)}$$

Applying KVL in mesh 3,

$$2i_3 + 2(i_3 - i_1) + 2(i_3 - i_2) = 0$$

$$\Rightarrow 2i_3 + 2i_3 - 2i_1 + 2i_3 - 2i_2 = 0$$


$$\Rightarrow \boxed{-2i_1 - 2i_2 + 6i_3 = 0} \quad \text{--- (III)}$$

Solving (I), (II) & (III),

$$\boxed{I_1 = I_S = 3.33 \text{ A}}$$

Problem 7

- Find i_o using mesh analysis.

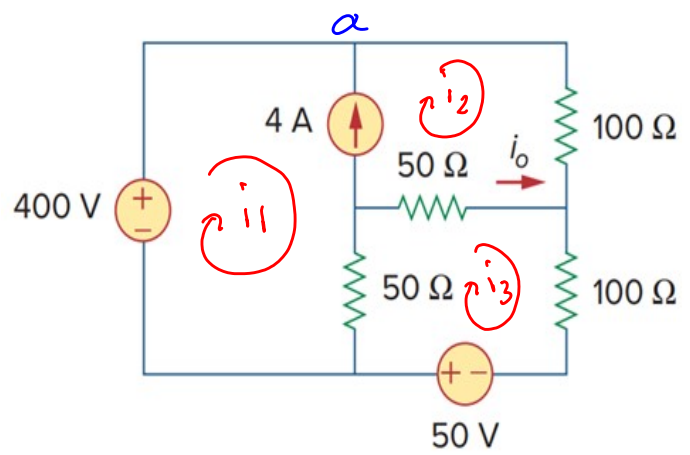

Applying KVL in mesh 3,

$$-50 + 50(i_3 - i_1) + 50(i_3 - i_2) + 100i_3 = 0$$

$$\Rightarrow -50 + 50i_3 - 50i_1 + 50i_3 - 50i_2 + 100i_3 = 0$$

$$\Rightarrow \boxed{-50i_1 - 50i_2 + 200i_3 = 50} \quad \text{--- (I)}$$

Applying KVL in supermesh of 1 & 2,

$$-400 + 100i_2 + 50(i_2 - i_3) + 50(i_1 - i_3) = 0$$

$$\Rightarrow -400 + 100i_2 + 50i_2 - 50i_3 + 50i_1 - 50i_3 = 0$$

$$\Rightarrow \boxed{50i_1 + 150i_2 - 100i_3 = 400} \quad \text{--- (II)}$$

Applying KCL at node a,

$$i_1 + 4 = i_2$$

$$\Rightarrow \boxed{i_1 - i_2 = -4} \quad \text{--- (III)}$$

Solving (I), (II), (III),

$$\boxed{i_1 = -0.5 \text{ A}}$$

$$\boxed{i_2 = 3.5 \text{ A}}$$

$$\boxed{i_3 = 1 \text{ A}}$$


$$i_o = i_3 - i_2$$

$$= 1 - 3.5$$

$$= \boxed{-2.5 \text{ A}}$$

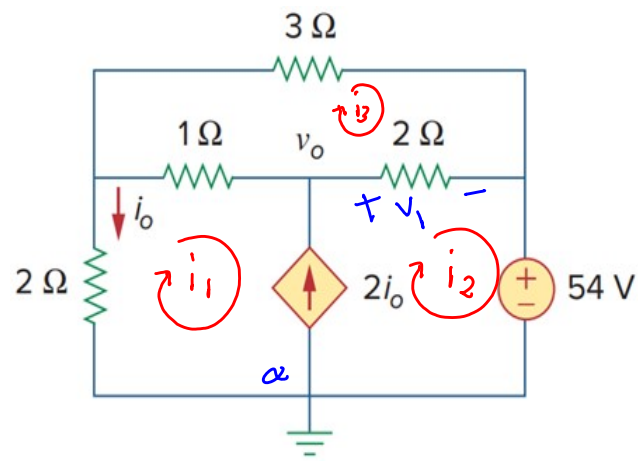Problem 8

- Find i_0 using mesh analysis. Determine the node voltage v_0 .



Applying KVL in mesh 1,

$$3i_3 + 2(i_3 - i_2) + 1 \cdot (i_3 - i_1) = 0$$

$$\Rightarrow 3i_3 + 2i_3 - 2i_2 + i_3 - i_1 = 0$$

$$\Rightarrow \boxed{-i_1 - 2i_2 + 6i_3 = 0} \quad \text{--- (I)}$$

Applying KVL in supermesh between mesh 1 & 2,

$$2i_1 + 1 \cdot (i_1 - i_3) + 2(i_2 - i_3) + 54 = 0$$

$$\Rightarrow 2i_1 + i_1 - i_3 + 2i_2 - 2i_3 + 54 = 0$$

$$\Rightarrow \boxed{3i_1 + 2i_2 - 3i_3 = -54} \quad \text{--- (II)}$$

Applying KCL at node a,

$$2i_0 + i_1 = i_2$$

$$\Rightarrow 2(-i_1) + i_1 = i_2$$

$$\Rightarrow \boxed{i_1 + i_2 = 0} \quad \text{--- (III)}$$

Solving (I), (II) & (III),

$$\boxed{i_1 = -36 \text{ A}}$$

$$\boxed{i_3 = 6 \text{ A}}$$

$$\boxed{i_2 = 36 \text{ A}}$$

$$\boxed{i_0 = 36 \text{ A}}$$

from the circuit,

$$V_o = V_1 + 54$$


$$\Rightarrow V_o = (i_2 - i_3)2 + 54$$

$$\Rightarrow V_o = (36 - 6) \times 2 + 54$$

$$\Rightarrow \boxed{V_o = 114 \text{ V}}$$

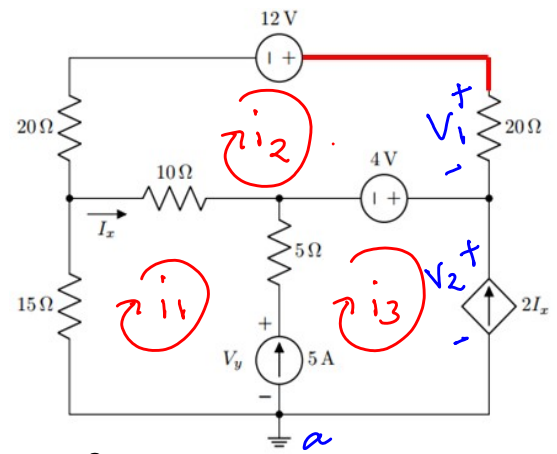Problem 9

- Use Mesh Analysis to analyze the circuit. Find V_y . Determine the red colored node voltage.



Applying KVL in mesh 2,

$$-12 + 20i_2 + 4 + 10(i_2 - i_1) + 20i_2 = 0$$

$$\Rightarrow -12 + 20i_2 + 4 + 10i_2 - 10i_1 + 20i_2 = 0$$

$$\Rightarrow \boxed{-10i_1 + 50i_2 = 8} \quad \text{--- (I)}$$

from circuit,

$$i_3 = -2I_x$$

$$I_x = (i_1 - i_2)$$

$$\therefore i_3 = -2(i_1 - i_2)$$

$$\Rightarrow i_3 = -2i_1 + 2i_2$$

$$\Rightarrow \boxed{2i_1 - 2i_2 + i_3 = 0} \quad \text{--- (II)}$$

Applying KCL in node a,

$$5 + i_1 = i_3$$

$$\Rightarrow \boxed{i_1 - i_3 = -5} \quad \text{--- (III)}$$

Solving (I), (II) & (III),

$$i_1 = -1.8 \text{ A}$$

$$i_2 = -0.2 \text{ A}$$

$$i_3 = 3.2 \text{ A}$$

To find V_y , Applying KVL in mesh 1,

$$15i_1 + 10(i_1 - i_2) + 5(i_1 - i_3) + V_y = 0$$

$$\Rightarrow 15 \times -1.8 + 10(-1.8 + 0.2) + 5(-1.8 - 3.2) + V_y = 0$$

$$\Rightarrow V_y = 68 \text{ V}$$

To find red marked node voltage, $V_o = V_1 + V_2$

$$V_1 = i_2 \times 20 = -0.2 \times 20 = -4 \text{ V}$$

To find, V_2 , we apply KVL in the mesh 3,

$$-V_y + 5(i_3 - i_1) - 4 + V_2 = 0$$

$$\Rightarrow -68 + 5(3.2 + 1.8) - 4 + V_2 = 0$$


$$\Rightarrow V_2 = 47 \text{ V}$$

$$\text{now, } V_o = V_1 + V_2 = 47 - 4$$

$$\Rightarrow V_o = 43 \text{ V}$$

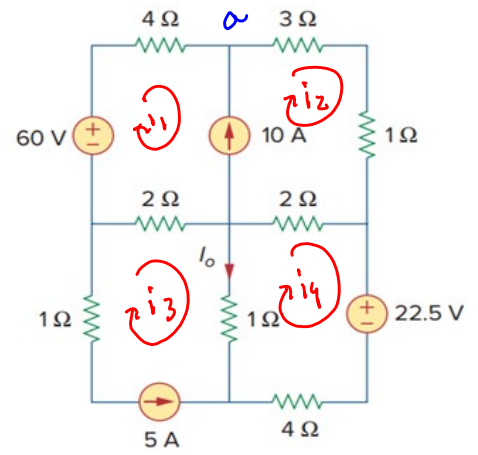Problem 10

- Derive the mesh equations for the following circuit. Determine i_o .



Here, $i_3 = -5A$

Applying KVL in mesh 4,

$$4i_4 + 1(i_4 - i_3) + 2(i_4 - i_2) + 22.5 = 0$$

$$\Rightarrow 4i_4 + i_4 + 5 + 2i_4 - 2i_2 + 22.5 = 0$$

$$\Rightarrow -2i_2 + 7i_4 = -27.5 \quad \text{--- (i)}$$

Applying KVL in supermesh between mesh 1 & 2,

$$-60 + 4i_1 + 3i_2 + 1 \cdot i_2 + 2(i_2 - i_4) + 2(i_1 - i_3) = 0$$

$$\Rightarrow -60 + 4i_1 + 3i_2 + i_2 + 2i_2 - 2i_4 + 2i_1 + 10 = 0$$

$$\Rightarrow 6i_1 + 6i_2 - 2i_4 = 50 \quad \text{--- (ii)}$$

Applying KCL at node a,

$$i_1 + 10 = i_2 \Rightarrow i_1 - i_2 = -10 \quad \text{--- (iii)}$$

Solving (i), (ii) & (iii),

$$i_1 = -1.06A$$

$$i_3 = -1.375A$$

$$i_2 = 8.94A$$


$$i_o = i_3 - i_4$$

$$\Rightarrow i_o = -5 - (-1.375)$$

$$\Rightarrow i_o = -3.625$$

Problem 11

- Find the mesh currents.

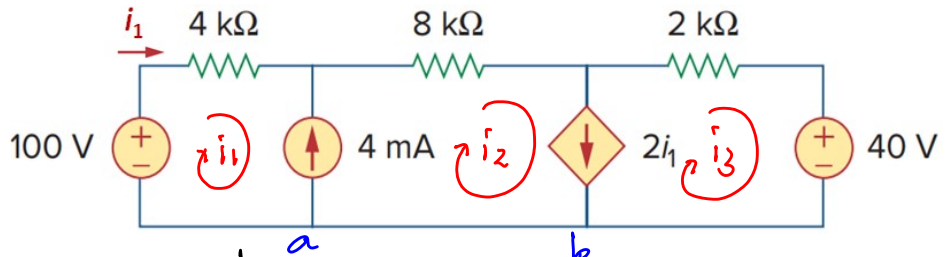

Applying KVL in the supermesh among 1, 2 & 3,

$$-100 + 4i_1 + 8i_2 + 2i_3 + 40 = 0$$

$$\Rightarrow 4i_1 + 8i_2 + 2i_3 = 60 \quad \text{--- (I)}$$

Applying KCL at node a,

$$i_1 + 4 = i_2$$

$$\Rightarrow i_1 - i_2 = -4 \quad \text{--- (II)}$$

Applying KCL at node b,

$$i_2 = 2i_1 + i_3$$

$$\Rightarrow 2i_1 - i_2 + i_3 = 0 \quad \text{--- (III)}$$

Solving (I), (II) & (III),

$$i_1 = 2 \text{ mA}$$

$$i_2 = 6 \text{ mA}$$

$$i_3 = 2 \text{ mA}$$

Problem 12

- (i) Use nodal analysis to find i_x . Determine the voltage across the 3 A source.
 (ii) Use mesh analysis to find i_x . Determine the voltage of the red colored node

Applying KVL in supermesh
among 1, 2 & 3

$$2i_1 + 6i_2 + 3i_3 = 0 \quad \text{--- (I)}$$

Applying KCL in node a,

$$i_1 + 3 = i_2$$

$$\Rightarrow i_1 - i_2 = -3 \quad \text{--- (II)}$$

Applying KCL in node b,

$$i_3 + 2i_x = i_1$$

$$\Rightarrow i_3 + 2(-i_1) = i_1$$

$$\Rightarrow 3i_1 - i_3 = 0 \quad \text{--- (III)}$$


Solving (I), (II) & (III),

$$i_1 = -1.059 \text{ A}$$

$$i_2 = 1.94 \text{ A}$$

$$i_3 = -3.176 \text{ A}$$

$$i_x = -i_1 = 1.059 \text{ A}$$

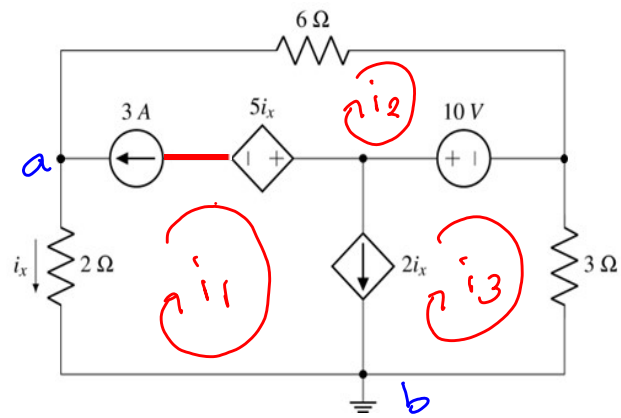

Applying KVL in mesh 2,

$$6i_2 - 10 + 5i_2 - V_1 = 0$$

$$\Rightarrow 6 \times 1.94 - 10 + 5 \times 1.059 - V_1 = 0$$

$$\Rightarrow \boxed{V_1 = 6.935 \text{ V}}$$

Problem 13

- Use mesh analysis to analyze the circuit. Find I_x .
- Determine the current I_y .

Applying KVL in mesh 1,

$$6i_1 + 12(i_1 - i_4) = 0$$

$$\Rightarrow 6i_1 + 12i_1 - 12i_4 = 0$$

$$\Rightarrow \boxed{18i_1 - 12i_4 = 0} \quad \text{--- (1)}$$

Applying KVL in mesh 4,

$$12(i_4 - i_1) + 3.5(i_4 - i_3) + 0.5(i_4 - i_5) + 14 = 0$$

$$\Rightarrow 12i_4 - 12i_1 + 3.5i_4 - 3.5i_3 + 0.5i_4 - 0.5i_5 + 14 = 0$$

$$\Rightarrow \boxed{-12i_1 - 3.5i_3 + 16i_4 - 0.5i_5 = -14} \quad \text{--- (11)}$$

Applying KVL in supermesh of 2, 3, 5


$$4i_2 + 0.5(i_5 - i_4) + 3.5(i_3 - i_4) = 0$$

$$\Rightarrow 4i_2 + 0.5i_5 - 0.5i_4 + 3.5i_3 - 3.5i_4 = 0$$

$$\Rightarrow \boxed{4i_2 + 3.5i_3 - 4i_4 + 0.5i_5 = 0} \quad \text{--- (111)}$$

Applying KCL at node a,

$$i_3 + 1 = i_2$$

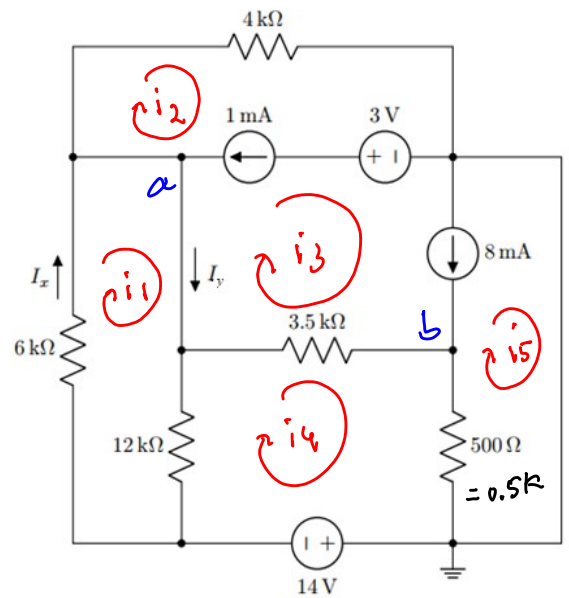

$$\Rightarrow i_2 - i_3 = 1 \quad \text{--- (iv)}$$

Applying KCL at node b,

$$i_5 + 8 = i_3$$

$$\Rightarrow i_3 - i_5 = 8 \quad \text{--- (v)}$$

Solving (i), (ii), (iii), (iv) & (v),

$$i_1 = -2 \text{ mA}$$

$$i_2 = -0.5 \text{ mA}$$

$$i_3 = -1.5 \text{ mA}$$

$$i_4 = -3 \text{ mA}$$

$$i_5 = -9.5 \text{ mA}$$

$$I_x = i_1 = -2 \text{ mA}$$

$$I_y = i_1 - i_3 = -2 - (-1.5)$$

$$I_y = -0.5 \text{ mA}$$

Problem 15

- Use mesh analysis to determine v_x and i_x . What is the voltage across the 3 A source?

Applying KVL in supernode among 1, 2, 3,

$$-50 + 10i_1 + 5i_3 + 4i_x = 0$$

$$\Rightarrow -50 + 10i_1 + 5i_3 + 4i_1 = 0$$

$$\Rightarrow \boxed{14i_1 + 5i_3 = 50} \quad \text{--- (i)}$$

Applying KVL at point a,

$$i_1 + 3 = i_2$$

$$\Rightarrow \boxed{i_1 - i_2 = -3} \quad \text{--- (ii)}$$


Applying KVL at point b,

$$i_2 + \frac{v_x}{4} = i_3$$

$$\text{where, } v_x = 2(i_1 - i_3)$$

$$\therefore i_2 + \frac{2(i_1 - i_3)}{4} = i_3$$
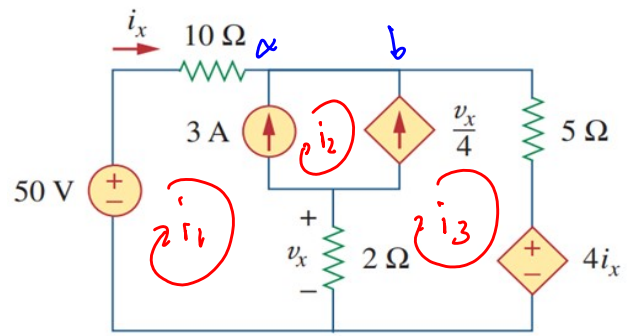
$$\Rightarrow i_2 + 0.5i_1 - 0.5i_3 = i_3$$



$$\boxed{i_x = i_1}$$

$$\Rightarrow 0.5i_1 + i_2 - 1.5i_3 = 0 \quad \text{--- (iii)}$$

Solving (i), (ii) & (iii),

$$i_1 = 2.105 \text{ A}$$

$$i_2 = 5.105 \text{ A}$$

$$i_3 = 4.105 \text{ A}$$

$$i_x = i_1 = 2.105 \text{ A}$$

$$\begin{aligned} V_x &= 2(i_1 - i_3) \\ &= 2(2.105 - 4.105) \end{aligned}$$

$$V_x = -4 \text{ V}$$

