

Assignment No-04

Name: Tahsin Raihan Rabbani


ID : 22201344

Course : CSE251


Section : 22.

Ans to the Q No-1


(a) I_D - V characterization of MOSFET.

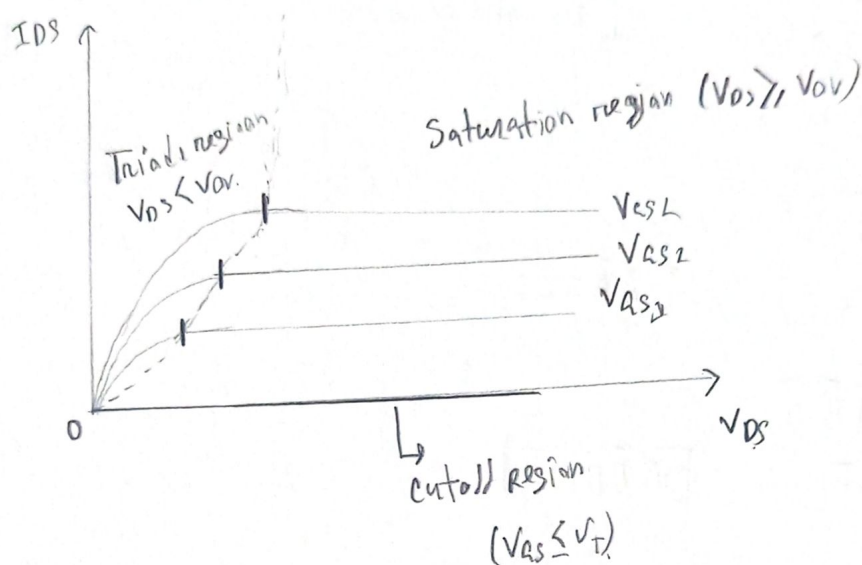


(b) NOR

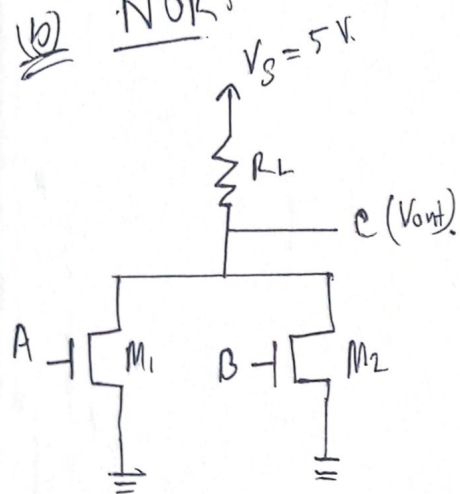

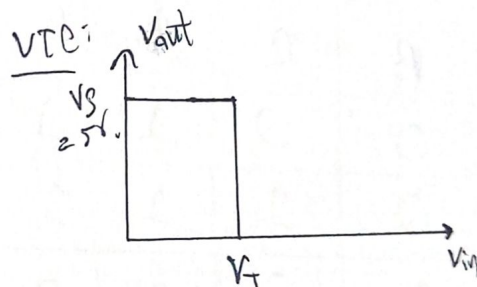when $A=0$
 $c=1$ for $B=0$
 $c=0$ for $B=1$



when $A=1$
 $c=0$ for $B=0$ and $B=1$

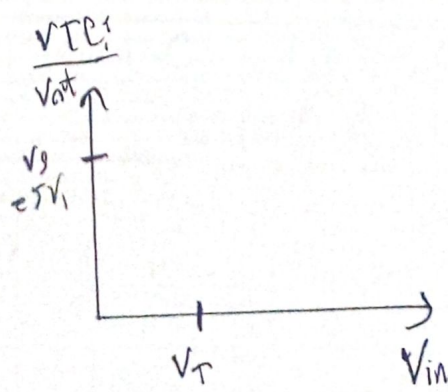

Truth table:

A	B	$c(V_{out})$
0	0	1 (5V)
0	1	0
1	0	0
1	1	0

(Q) $Z = \overline{(A + \bar{A}B + BC)}$

$$= \bar{A} (\bar{A} + \bar{B}) (\bar{B} + \bar{C})$$

[De Morgan's law]

$$= \bar{A} (A + \bar{B}) (\bar{B} + \bar{C})$$

$$= (\bar{A}\bar{A} + \bar{A}\bar{B}) (\bar{B} + \bar{C})$$

$$= (0 + \bar{A}\bar{B}) (\bar{B} + \bar{C})$$

[$\bar{A}\bar{A} = 0$]

$$= \bar{A}\bar{B}\bar{B} + \bar{A}\bar{B}\bar{C}$$

$$= \bar{A}\bar{B} + \bar{A}\bar{B}\bar{C}$$

[$\bar{B}\bar{B} = \bar{B}$]


$$\therefore Z = \bar{A}\bar{B}$$

[$A + A\bar{B} = A$]

Truth table:


A	B	C	$\bar{A}$	$\bar{B}$	Output
0	0	0	1	1	1
0	0	1	1	1	1
0	1	0	1	0	0
0	1	1	1	0	0
1	0	0	0	1	0
1	0	1	0	1	0
1	1	0	0	0	0
1	1	1	0	0	0

(b) $X = \overline{A}\overline{B} + AB$

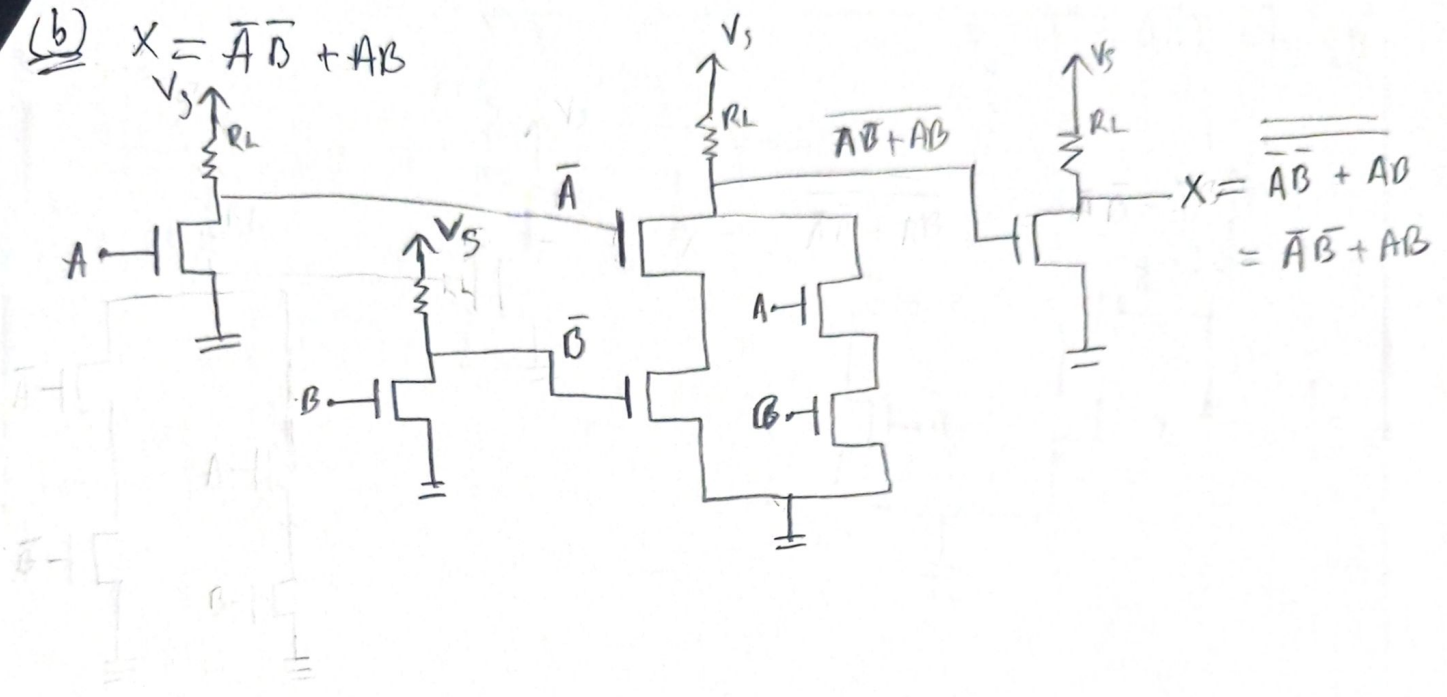


Ans to the Q No-3


(a) $L = (A+B)C$

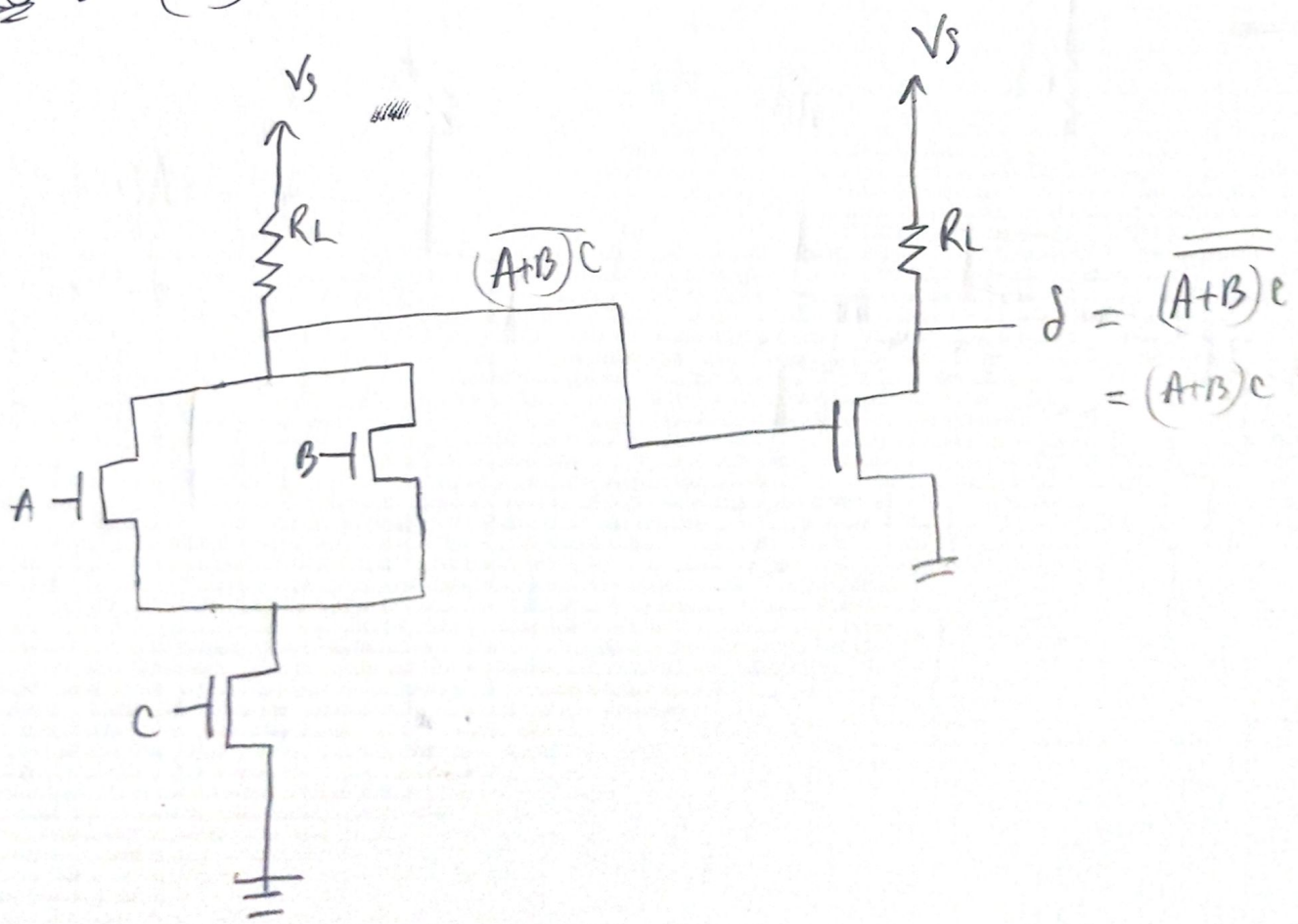

(b) $f = (\bar{A}B + CD)$

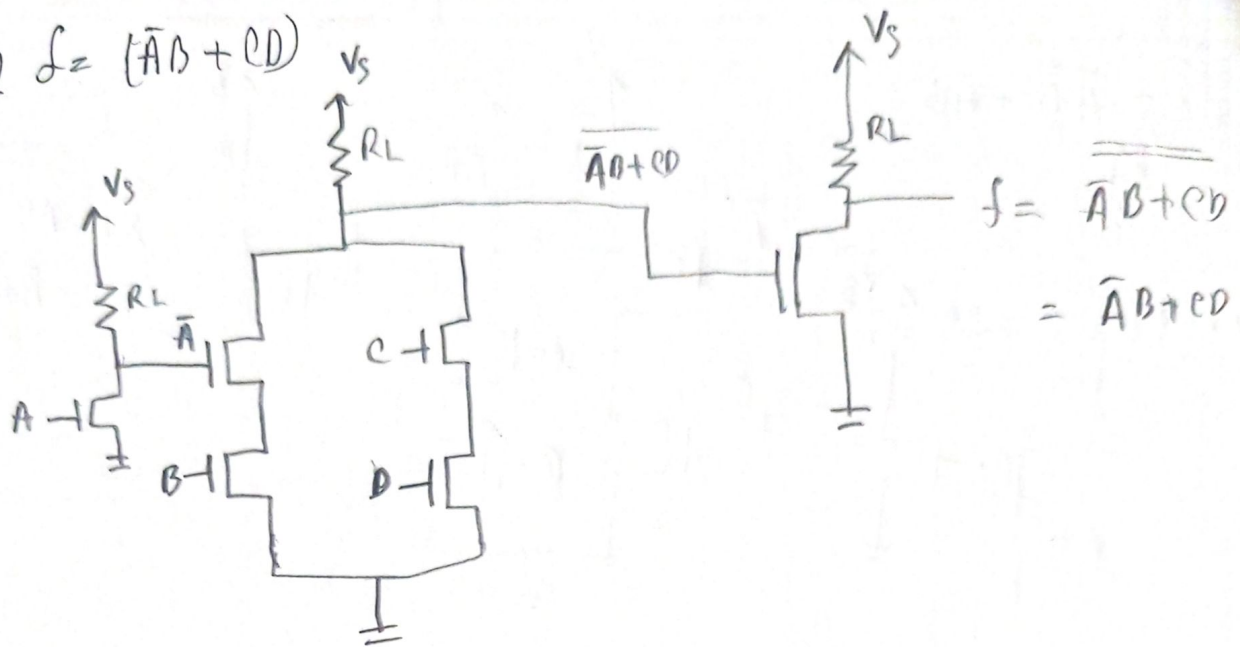

(c) $f = AB + A + CD$

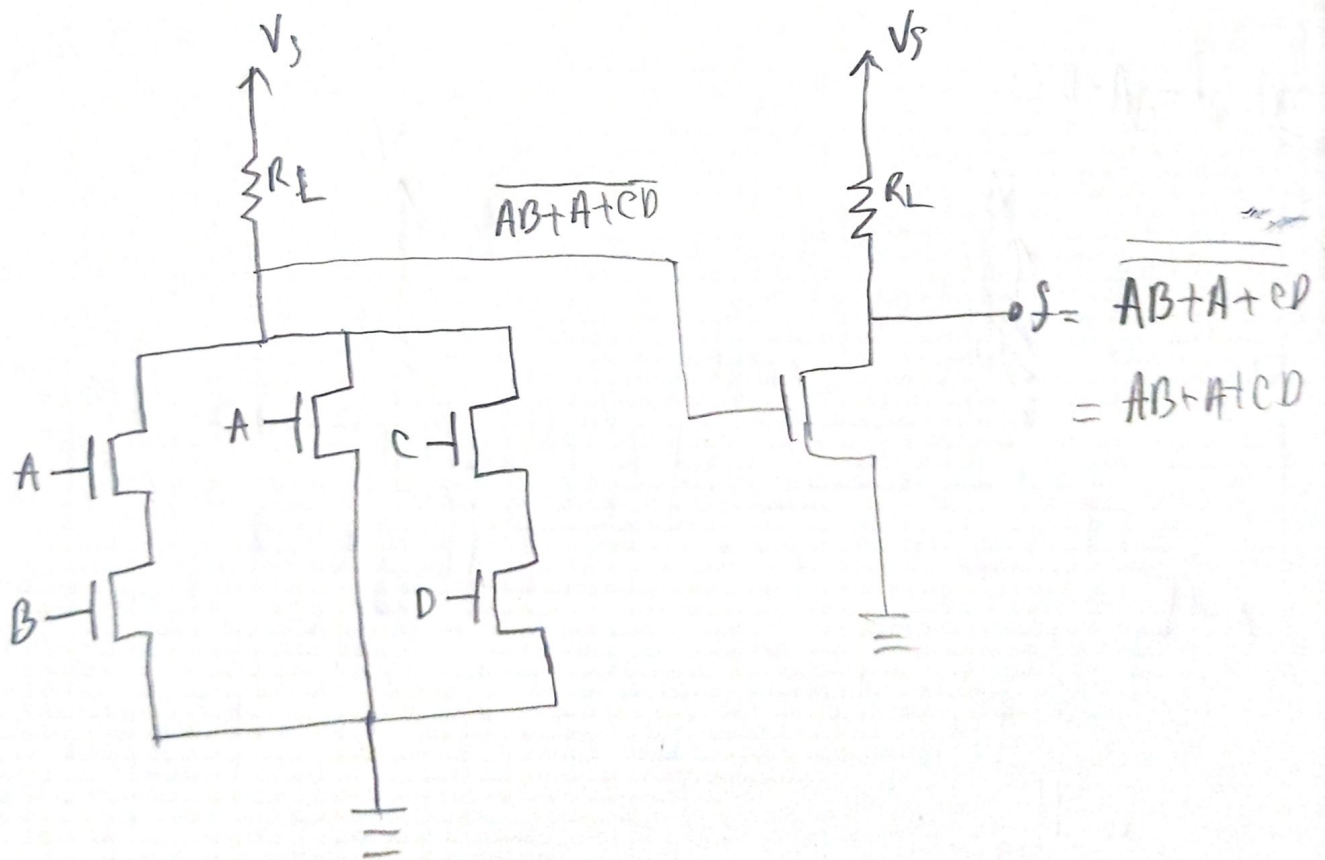

Here,

Ans to the Q No-4

3

$$V_t = 1, \quad V_G = 4V, \quad i_{DS} = 2mA, \quad k = 4mA/V^2$$

$$\text{So } i_{DS} = \frac{10 - V_D}{1}$$

$$\Rightarrow V_D = 10 - 2 = 8V,$$

Assume the MOSFET is in saturation mode, so, $V_{DS} \geq V_{GS} - V_t$

$$i_{DS} = \frac{k}{2} [V_{GS} - V_t]^2$$

$$\Rightarrow 2 = \frac{4}{2} [V_G - V_S - V_t]^2$$

$$\Rightarrow 2 = 2 [4 - V_S - 1]^2$$

$$\Rightarrow V_S^2 - 6V_S - 8 = 0$$

$$\Rightarrow V_S = 4 \text{ or } 2.$$

$$V_S = 4 \text{ [not possible]} \quad \text{so } V_S = 2V.$$

Verify:

$$V_{DS} = V_D - V_S = 8 - 2 = 6V$$

$$V_{GS} = V_G - V_S = 2V.$$

$$V_{GS} - V_t = 2 - 1 = 1V.$$

Here $V_{DS} \geq V_{GS} - V_t$ so the MOSFET is in saturation mode.

$\therefore$ Assumption correct.

Ans

Ans to the Q No-5

(i) $E=2$, $V_T=0.3$, $K_n=0.1 \text{ mA/V}^2$

For M1:

$$V_1 = \frac{3}{9} \times 5$$

$$= 1.67 \text{ V}$$

$$V_G = 1.67 \text{ V}, \quad V_S = 0 \text{ V}$$

$$V_{GS} = 1.67 \text{ V}$$

$$\therefore V_{GS} > V_T$$

Here, $V_D = 5 \text{ V}$

$$V_{DS} = 5 \text{ V}$$

Now,

$$V_{OV} = V_{GS} - V_T = 1.67 - 0.3 = 1.37 \text{ V}$$

Here $V_{DS} > V_{OV}$

$\therefore$ M1 is in saturation mode,

$$\therefore i_{D1} = \frac{K}{2} [V_{OV}]^2 = \frac{0.1}{2} [1.37]^2 = 0.0938 \text{ mA}$$


Ans

For M2:

$$V_2 = \frac{6}{9} \times 5 = 3.33 \text{ V} \quad [\text{Voltage divider rule}]$$

$$\therefore V_G = 3.33 \text{ V}, \quad V_D = 5 \text{ V}, \quad V_T = 0.3 \text{ V} \quad K = 0.1 \text{ mA/V}^2$$

Let's assume M2 is in saturation mode,

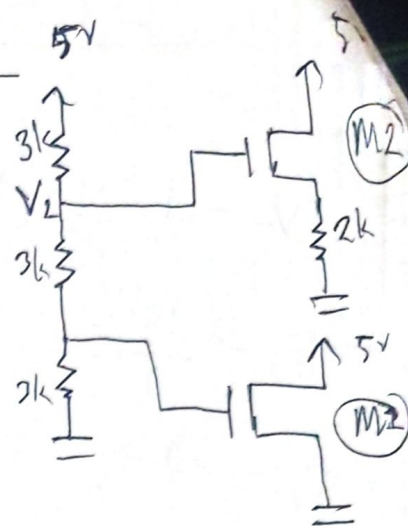

we know

$$i_{D_S} = \frac{k}{2} [V_{GS} - V_T]^2$$

$$\frac{V_S}{2} = \frac{0.1}{2} [V_{GS} - V_T]^2$$

$$\frac{V_S}{2} = [3.33 - V_S - 0.3]^2 \times \frac{0.1}{2}$$

$$V_S = (9.18 - 6.06V_S + V_S)^2 \times 0.1$$

$$V_S = 0.918 - 0.606V_S + 0.1V_S^2$$

$$0.1V_S^2 - 1.606V_S + 0.918 = 0$$

$$V_S = 15.46 \text{ V or } 0.59 \text{ V}$$

So $V_S = 0.59 \text{ V}$ [$V_S = 15.46$ not possible]

$$\therefore V_{GS} = 3.33 - 0.5 = 2.74 \text{ V}$$

$$\therefore \boxed{V_{GS} > V_T}$$

$$\text{Now } V_{DS} = V_D - V_S = 5 - 0.59 = 4.41 \text{ V}$$

$$V_{DS} = V_{GS} - V_T = 2.74 - 0.3 = 2.44 \text{ V}$$

$$\therefore \boxed{V_{DS} > V_{DS}} \text{ (Note: likely intended } V_{DS} > V_{GS} - V_T \text{)}$$

So assumption correct. It is in saturation mode.

$$\therefore P_{2k\Omega} = V_S I_S$$

$$= 0.59 \times \frac{0.1}{2}$$

$$= 0.175 \text{ mW}$$

Ans

$$\begin{cases} i_{D_S} = I_S = I_{OS} \\ i_S = \frac{V_S - 0}{2} = \frac{V_S}{2} \end{cases}$$

Q1 $E = 5$, $V_T = 0.3V$, $K_n = 0.1 \text{ mA/V}^2$

For M1:

$$V_1 = \frac{3}{9} \times 11 = 3.67V \quad [\text{voltage divider rule}]$$

$\therefore V_G = 3.67V$, $V_S = 0V$

$\therefore V_{GS} = 3.67V$

$\therefore \boxed{V_{GS} > V_T}$

Now, $V_D = 5V$.

$V_{DS} = 5V$,

So, $\boxed{V_{DS} > V_{ov}}$

$\therefore$ M1 transistor is in saturation mode.

$\therefore I_{DS} = \frac{K}{2} [V_{ov}]^2 = \frac{0.1}{2} [3.37]^2 = 0.57 \text{ mA}$

For M2:

$$V_2 = \frac{6}{9} \times 11 = 7.33V$$

$\therefore V_G = 7.33V$, $V_D = 5V$, $V_T = 0.3V$, $K_n = 0.1 \text{ mA/V}^2$. Let's assume

M2 transistor is in triode mode.

So $i_{DS} = K [V_{GS} - V_T - \frac{1}{2} V_{DS}] V_{DS}$


$i_{DS} = \frac{V_S}{2}$

$\therefore i_{DS} = K (V_G - \frac{1}{2} V_S - V_T - \frac{1}{2} V_D) \cdot (V_D - V_S)$

$\therefore i_{DS} = K (7.33 - \frac{1}{2} V_S - 0.3 - \frac{1}{2} \times 5) (5 - V_S)$

$\therefore i_{DS} = K (22.65 - \frac{5}{2} V_S - 4.53 V_S + \frac{1}{2} V_S^2)$

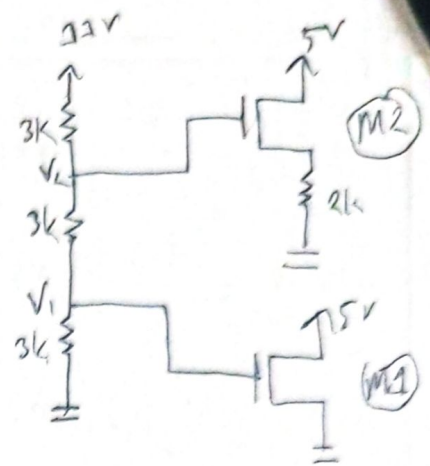$\therefore \frac{V_S}{2} = 0.1 \left(\frac{1}{2} V_S^2 - 7.03 V_S + 22.65 \right)$



$$V_S = 0.2 \left(\frac{1}{2} V_S^2 - 7.03 V_S + 22.65 \right)$$

$$= 0.1 V_S^2 - 2.406 V_S + 4.53 = 0$$

$$\text{So, } V_S = 22 \text{ V or } V_S = 2.05 \text{ V.}$$

[$V_S = 22 \text{ V}$ not possible]

$$\text{So, } V_{GS} = 7.33 - 2.05 = 5.28 \text{ V}$$

[$\therefore V_{GS} > V_T$]

$$V_{DS} = 5 - 2.05 = 2.95 \text{ V}$$

$$V_{ov} = 5.28 - 0.3 = 4.98 \text{ V}$$

$$\therefore V_{DS} < V_{ov} \quad [\text{Assumption is correct}]$$

$$P_{2kn} = V_S I_S = \left(2.05 \times \frac{2.05}{2} \right) = 2.11 \text{ mW.} \quad \underline{\text{Ans}}$$

Ans to the Q. No 6

(a) Condition to verify the saturation mode of a MOSFET are

i) $V_{GS} > V_T$ and ii) $V_{DS} \geq V_{ov}$

$k = 1 \text{ mA/V}^2$

(b) Here, $V_G = 5 \text{ V}$, $V_T = 1 \text{ V}$, $V_S = 0 \text{ V}$,

$$V_{GS} = 5 \text{ V. So, } \boxed{V_{GS} > V_T}$$

Let's assume MOSFET is in saturation mode;

$$I_{DS} = \frac{k}{2} [V_{ov}]^2$$

$$= \frac{10 - V_D}{0.1} = \frac{1}{2} [5 - 1]^2$$

$$\therefore V_D = 10 - 3.2 = 6.8 \text{ V.}$$

$$I_{DS} = \frac{10 - V_D}{0.1}$$

$$\therefore V_{DS} = 6.8 \text{ V}$$

$$V_{ov} = 5 - 1 = 4 \text{ V}$$

So, $V_{DS} > V_{ov}$ Assumption correct

$$\therefore V_{out} = 6.8 \text{ V}$$

Nirmal told the inverter will malfunction. As $V_D = 6.8 > 5$. So the output was high when input was high. So it malfunctioned. Nirmal was right.

(Am)

(C) Here, $V_G = 5 \text{ V}$, $V_S = 0 \text{ V}$, $V_T = 1 \text{ V}$, $R_D = 1 \text{ k}\Omega$

$$\therefore V_{GS} = 5 \text{ V}, \quad V_{ov} = 5 - 1 = 4 \text{ V}$$

$\therefore [V_{GS} > V_T]$ Let's assume it's in triode mode,

$$\text{So, } i_{D3} = K_D [V_{GS} - V_T - \frac{1}{2} V_{DS}] V_{DS}$$

$$\begin{cases} V_{DS} = V_D \\ i_{D3} = I_{D1} - i_{D2} \end{cases}$$

$$\therefore 10 - V_D = 4 \left[5 - 1 - \frac{1}{2} V_D \right] V_D$$

$$\therefore 10 - V_D = 16 V_D - 2 V_D^2$$

$$\therefore 2 V_D^2 - 17 V_D + 10 = 0$$

$$\therefore V_D = 7.86 \text{ V or } V_D = 0.63 \text{ V}$$

$$\text{We take } V_D = 0.63 \text{ V}$$

$$\therefore V_{DS} = 0.63 \text{ V}$$

$$\therefore V_{DS} < V_{ov}$$

[Assumption correct]

The inverter is working properly after modification.

⑥

Ans)

1d) $V_G = 5, V_S = 0, V_T = 1,$

$$V_{ov} = 5 - 1 = 4V.$$

At the edge of saturation, $V_{DS} = V_{ov}.$

$$\therefore V_{DS} = 4V, \quad \text{so, } V_{DS} = V_D = 4V.$$

$$\text{Now } I_{D1} = \frac{k}{2} [V_{ov}]^2 = \frac{4}{2} [4]^2 = 32 \text{ mA}$$

$$\text{So, } I_{DS} = \frac{10 - V_D}{R_D}$$

$$\therefore R_D = \frac{10 - V_D}{I_{DS}}$$

$$\therefore R_D = \frac{10 - 4}{32 \times 10^{-3}}$$

$$\therefore R_D = 187.5 \Omega.$$

$$\therefore R_D = 0.1875 \text{ k}\Omega.$$

$\therefore$ When $R_D = 0.1875 \text{ k}\Omega$ the MOSFET operates at the edge of saturation.

Ans)