

Assignment No-05

Name: Tahsin Raihan Rabbani

Id : 22201344

Course : CSE251.

Section : 22.

(1)

Assume active region,

Ans to the Q No-1We have to verify $V_{CE} > 0.2$, $V_{BE} = 0.7$, $I_C = \beta I_B$, $I_C \approx I_E$ Using KVL, $22 = 39I + 0.7 + 1.5I_E$

$$\Rightarrow 22 = 39I + 0.7 + 1.5(141)I_B$$

$$\Rightarrow 39I + 211.5I_B = 21.3 \quad \text{--- (i)}$$

$$\begin{cases} \beta I_B = I_C \\ I_E = I_B + I_C \\ \Rightarrow I_E = (1 + \beta)I_B \end{cases} \quad \frac{\beta}{\alpha} I_B$$

Now Using KVL, $22 = 39I + 39I_1$

$$\Rightarrow 22 = 39I + 39(I - I_B)$$

$$\Rightarrow 22 = 39 + 3.9I - 3.9I_B$$

$$\Rightarrow 42.9I - 3.9I_B = 22 \quad \text{--- (ii)}$$

Solving equation (i) & (ii), $I = 0.51 \text{ mA}$ & $I_B = 6.04 \mu\text{A}$.

$$\text{Now, } I_C = 140 \times 6.04 = 0.845 \text{ mA}$$

$$I_E = 141 \times 6.04 = 0.852 \text{ mA}$$


Now, Using KVL

$$22 = I_C R_C + V_{CE} + I_E R_E$$

$$\Rightarrow V_{CE} = 22 - (0.845 \times 10) - (0.852 \times 1.5) = 12.272 \text{ V}$$

As $V_{CE} > 0.2$ [Assumption correct]

$$\text{So, } V_{CE} = 12.272 \text{ V and } I_C = 0.845 \text{ mA}$$

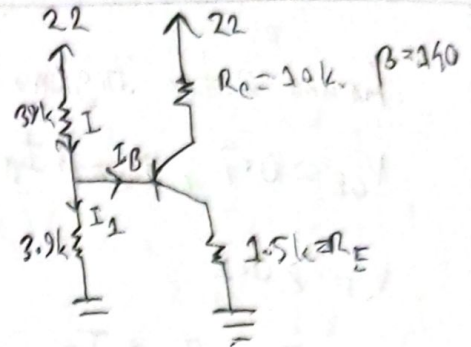Ans

Ans to the Q No-2

Assume active region,

$V_{BE} = 0.7$, $I_C = \beta I_B$ and we have to verify

$$V_{CE} > 0.2.$$

Now, $I = I_B + I_C$

Using KVL, $10 = 15I + 10I_B + V_{BE} + 5I_E - 10$,

$$\Rightarrow 10 = 15(I_B + I_C) + 10I_B + 0.7 + 5(1 + \beta)I_B - 10.$$

~~$$19.3 = 15I_B + 15\beta I_B + 10I_B + 5I_B + 5\beta I_B$$~~

$$\Rightarrow 19.3 = 15I_B + 1500I_B + 10I_B + 5I_B + 500I_B,$$

$$\Rightarrow 2030I_B = 19.3$$

$$\Rightarrow I_B = 9.507 \times 10^{-3} \text{ mA}$$

Now,

$$I_C = 100 \times 9.507 \times 10^{-3} = 0.95 \text{ mA}$$


$$I_E = 101 \times 9.507 \times 10^{-3} = 0.96 \text{ mA}$$

So, $I = 9.507 \times 10^{-3} + 0.95 = 0.96 \text{ mA}$.

Now,

$$\frac{10 - V_E}{15} = 0.96$$

$$\therefore V_E = -4.4 \text{ V}$$

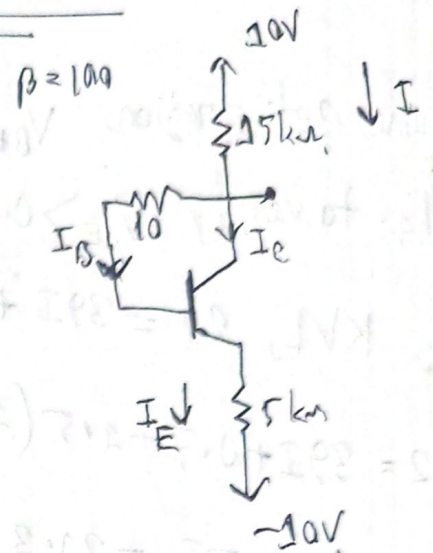

Now, $\frac{V_E + 10}{5} = 0.96$

$\Rightarrow V_E = -5.2 \text{ V}$

$\therefore V_{CE} = V_C - V_E = -4.4 - (-5.2) = -4.4 + 5.2 = 0.8 \text{ V}$

As $V_{CE} > 0.2$, no assumption correct.

So, $I_C = 0.95 \text{ mA}$ and $V_C = -4.4 \text{ V}$ Ans

Ans to the Q No-3

Here, $I_C = 2 \text{ mA}$ assume it is in active region,

$V_{BE} = 0.7$ and we have to verify $V_{CE} > 0.2$.

Now $\frac{15 - V_C}{R_C} = 2$ $\left[\frac{15 - V_C}{R_C} = I_C \right]$


$\Rightarrow R_C = 5 \text{ k}\Omega$

Now, $I_C = \beta I_B$

$\therefore I_B = \frac{I_C}{\beta}$

$\therefore I_B = \frac{2}{100}$

$\therefore I_B = 0.02 \text{ mA}$

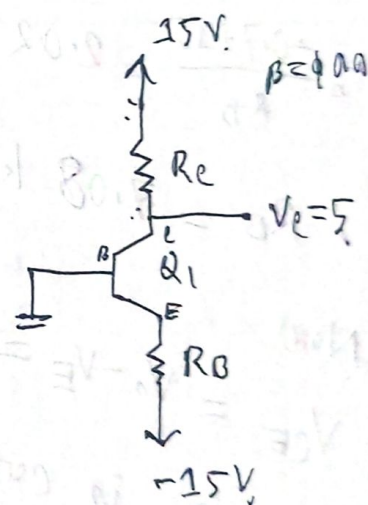

Now, $I_E = (1+\beta) I_B = 101 \times 0.02 = 2.02 \text{ mA}$.

Ass. $V_B = 0 \text{ V}$.

$V_{BE} = 0.7$.

$\therefore V_B - V_E = 0.7$,

$\therefore V_E = -0.7$.

Now

$$\frac{V_E - (-15)}{R_B} = I_E$$

$$\therefore \frac{-0.7 + 15}{R_B} = 2.02$$

$\therefore R_B = 7.08 \text{ k}\Omega$.

Now

$V_{CE} = V_C - V_E = 5 + 0.7 = 5.7$ which is greater than 0.2 . So our assumption is correct.

So,

$R_C = 5 \text{ k}\Omega$,

$R_B = 7.08 \text{ k}\Omega$.

Ans)

Assume active mode, so, Ans to the Q No-4
 $V_{BE} = 0.7$ no we have to verify $V_{CE} > 0.2$.

How,
 $I_E = 0.5 \text{ mA}$

$$I_C = \alpha I_E$$

$$I_C = \frac{\beta}{1+\beta} I_E$$

$$I_C = \frac{75}{76} \times 0.5$$

$$I_C = 0.493 \text{ mA}$$

So,
 $I_B = \frac{0.493}{75} = 6.573 \times 10^{-3} \text{ mA}$


Now
 $\frac{5 - V_C}{R_C} = I_C$

$$R_C = \frac{5 - 1}{0.493}$$

$$R_C = 8.113 \text{ k}\Omega$$

Now,
 $\frac{0 - V_B}{25} = 6.57 \times 10^{-3}$

$$V_B = -0.16425 \text{ V}$$

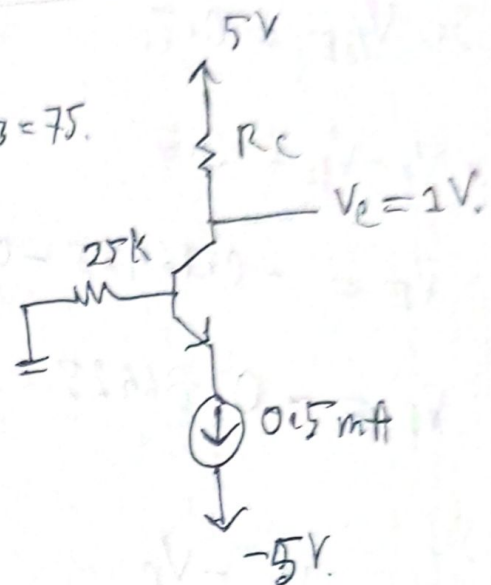

$$\text{So, } V_{BE} = 0.7.$$

$$\bullet V_B - V_E = 0.7.$$

$$\approx V_E = -0.16425 - 0.7.$$

$$\approx V_E = -0.86425 \text{ V.}$$

So,

$$V_{CE} = V_C - V_E$$

$$= 1 - (-0.86425)$$

$$= 1 + 0.86425$$

$$= 1.86425 \text{ V.}$$

So,

$V_{CE} > 0.2$ assumption is correct.

$$R_C = 8.113 \text{ k}\Omega.$$

(Am)