

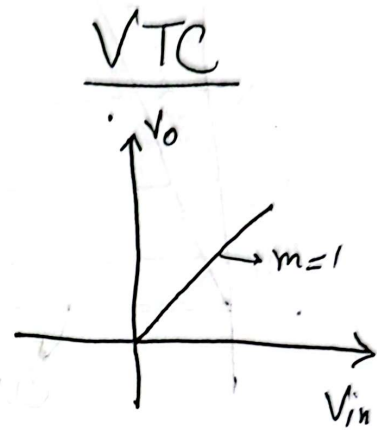
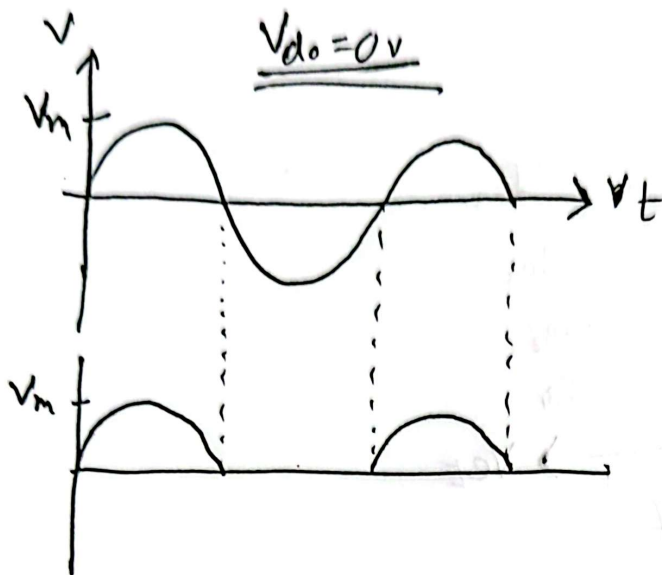


Half Wave Rectifier


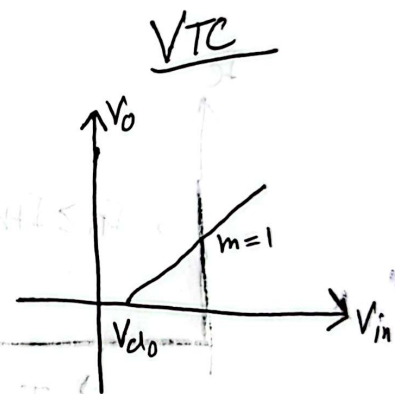


$$V_D = V_{D0}$$

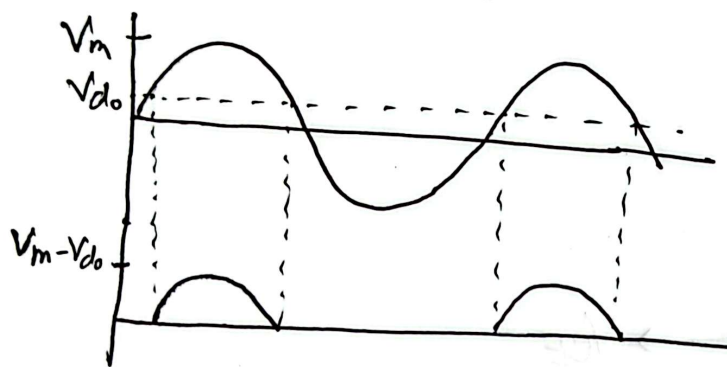


Full Wave Rectifier

$$V_D = V_{D0}$$

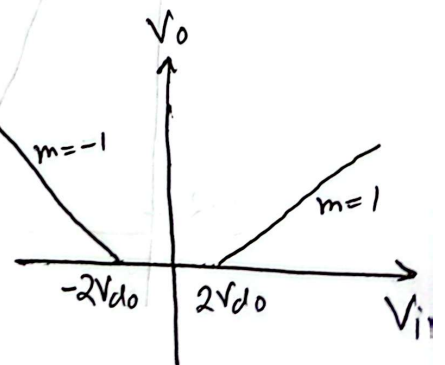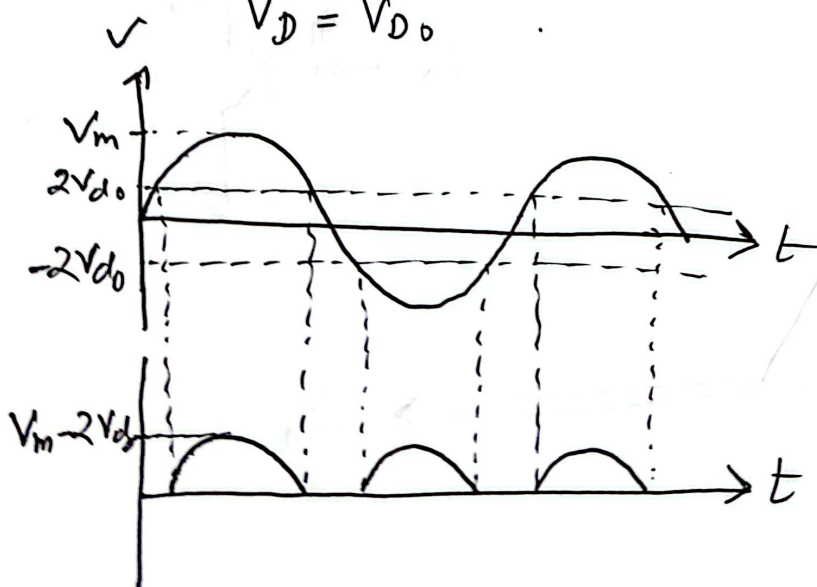


BJT

I-V I_c

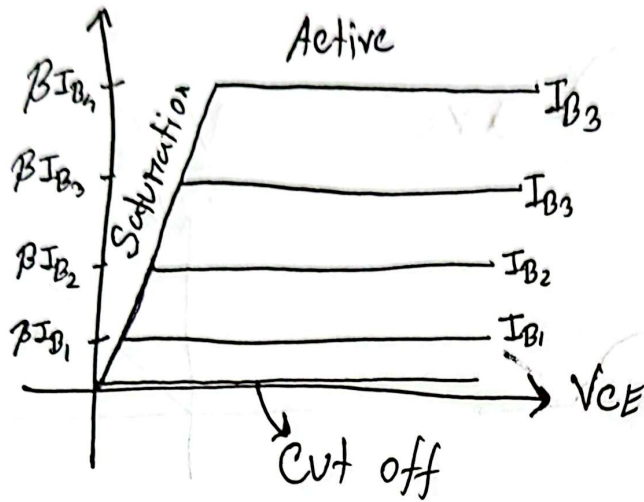

S-Model

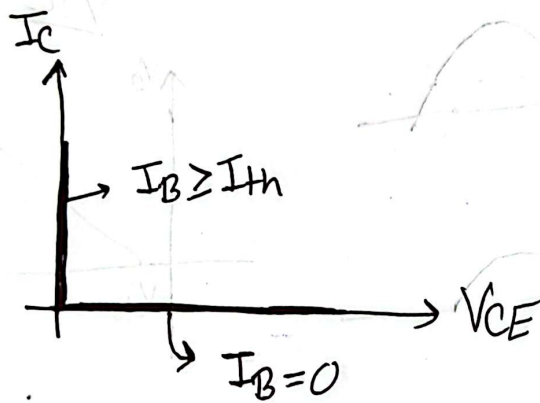

VTE of an inverter (BJT)

