

BRAC UNIVERSITY
Department of Computer Science and Engineering

Quiz 03
Semester: Fall 2024

Time: 15min
Full Marks:15

Name:	ID:	Section:
--------------	------------	-----------------

CSE 251: Electronic Devices and Circuits

1. [CO2] Consider a full wave rectifier with a load resistance of $R = 1 \text{ k}\Omega$ and a capacitor of $10 \mu\text{F}$ connected in parallel with the load . The rectifier is fed by an input V_i . The average current flowing through the load is 3 mA and the output frequency is 200 Hz.
[assume $V_{DO} = 1\text{V}$ for each diode]
 - a. Draw the rectifier circuit. 4
 - b. Determine the input equation of the waveform V_i . 7
 - c. Show the input and output waveforms with proper labeling 4

