

BRAC UNIVERSITY
Department of Computer Science and Engineering

Quiz 05
Semester: Fall 2024

Time: 25 min
Full Marks: 20

Name:	ID:	Section:
--------------	------------	-----------------

CSE 251: Electronic Devices and Circuits

1. [CO1] 5
Show the I-V characteristics graph of BJT (I_c vs V_{CE}) . **Identify** the operating regions in the graph.
2. [CO3] Implement the logic function, $f = \overline{\overline{(A + B)} \cdot \overline{C} \cdot D}$ using BJTs. 5

3. [CO2]

10

Analyze the following circuit to determine all node voltages, branch currents and R_C . Assume $\beta = 75$. You must validate your assumptions.

