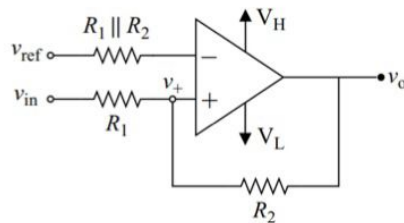


Question 1


For the Given Schmitt Trigger Circuit, $V_H = 10V$, $V_L = -10V$, $V_{ref} = 1V$




(a)	Is this an Inverting or non-inverting Schmitt Trigger?	1
(b)	Let $R_1 = 1 \text{ k}\Omega$, $R_2 = 2 \text{ k}\Omega$; Draw V_{out} vs. V_{in} graph (VTC) or Transfer curve with appropriate labels.	2
(c)	Let input voltage be 18V peak to peak sine wave. Draw V_{out} vs. time plot for the given input.	2

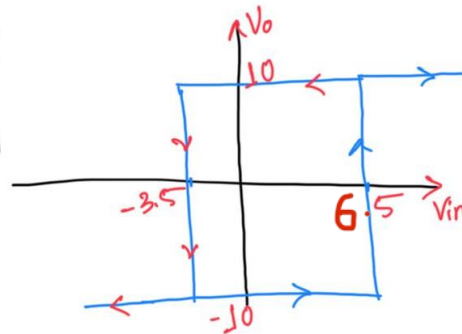(a) Non-Inverting


$$\begin{aligned}
 (b) \quad V_{UT} &= \left(-\frac{R_1}{R_2}\right)V_L + \frac{R_1 + R_2}{R_2}V_{ref} \\
 &= -\frac{1}{2}(-10) + \frac{3}{2} \times 1 \\
 &= 5 + 1.5 = 6.5 \\
 V_{LT} &= -5 + 1.5 = -3.5
 \end{aligned}$$



(c)

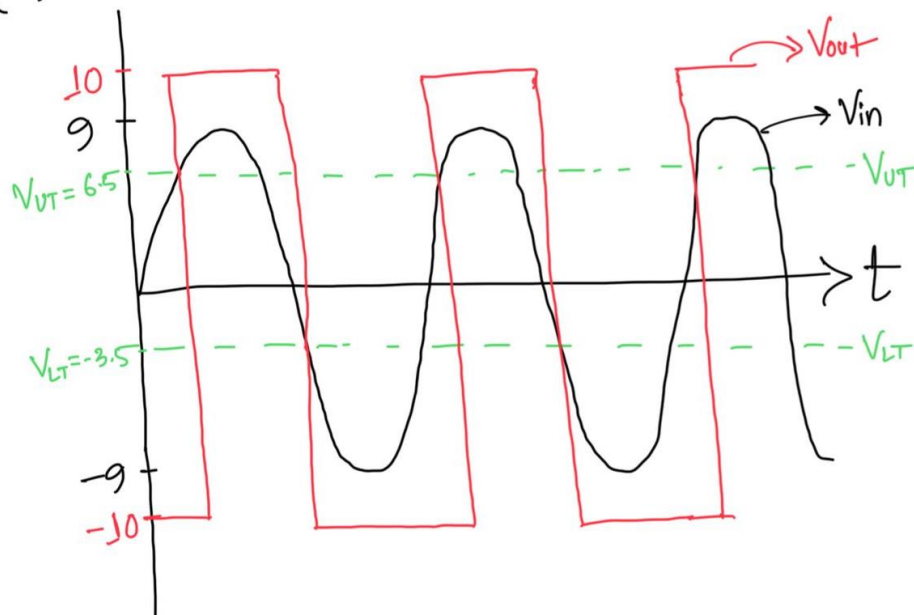


Question 3

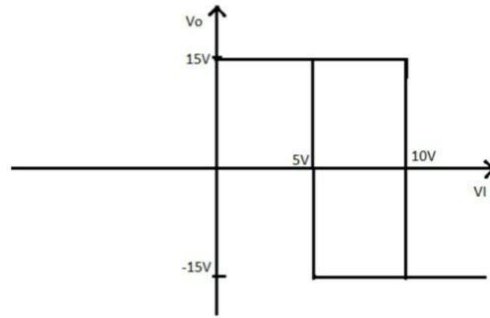

(a)	Identify the Schmitt trigger circuit from the VTC and also find out V_H , V_L , V_{UT} , V_{LT} , V_{shift}	2.5
(b)	Design a Schmitt trigger circuit that will produce the same VTC.	2.5

7.2) This is inverting schmitt trigger with V_{REF} .

$$\begin{aligned}
 V_H &= 15V, \\
 V_L &= -15V \\
 V_{TH} &= +10V \\
 V_{TL} &= +5V \\
 V_{Hysteresis} &= V_{TH} - V_{TL} = 5V \\
 V_S &= \frac{V_{TH} + V_{TL}}{2} = \frac{10 + 5}{2} = 7.5
 \end{aligned}$$

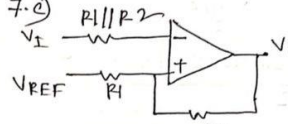7.2) 

$$V_S = V_{REF} \times \frac{R_2}{R_1 + R_2} \rightarrow (1)$$

$$V_{Hysteresis} = (V_H - V_L) \times \frac{R_1}{R_1 + R_2} \rightarrow (2)$$

We know, from graph
 $V_S = 7.5V$
 $V_{Hysteresis} = 5V$

From (1), $5 = (15 + 15) \times \frac{R_1}{R_1 + R_2}$

$$\frac{R_1}{R_1 + R_2} = \frac{1}{6} \Rightarrow \frac{R_1}{R_2} = \frac{1}{5}$$

ULKASEMI
We are Integrating your Ideas

web: www.ulkasemi.com
e-mail: info@ulkasemi.com

CS CamScanner

Now suppose, $R_1 = 1k\Omega$,

$$\begin{aligned}
 \text{then, } \frac{1k}{R_2} &= \frac{1}{5} \\
 R_2 &= 5k\Omega
 \end{aligned}$$

From (1), $7.5 = V_{REF} \times \frac{5}{1 + 5}$

$$\Rightarrow V_{REF} = +9V$$

~~XXXXXXXXXX~~ Qus - 3

(a) $R_1 = R_2$, $V_H = 8V$, $V_L = -8V$, $C_x = 100nF$
 $f = 200Hz$, $T = \frac{1}{200} = 5ms$, $D = 0.5$


$\therefore T_1 = DT = 2.5ms$

$V_{UT} = \frac{R_1}{R_1 + R_2} V_H = 4V$, $V_{LT} = \frac{R_1}{R_1 + R_2} V_L = -4V$

$T_1 = R_x C_x \ln \left| \frac{V_H - V_{LT}}{V_H - V_{UT}} \right|$

$2.5 \times 10^{-3} = R_x \times 100 \times 10^{-9} \ln \left| \frac{8 + 4}{8 - 4} \right|$

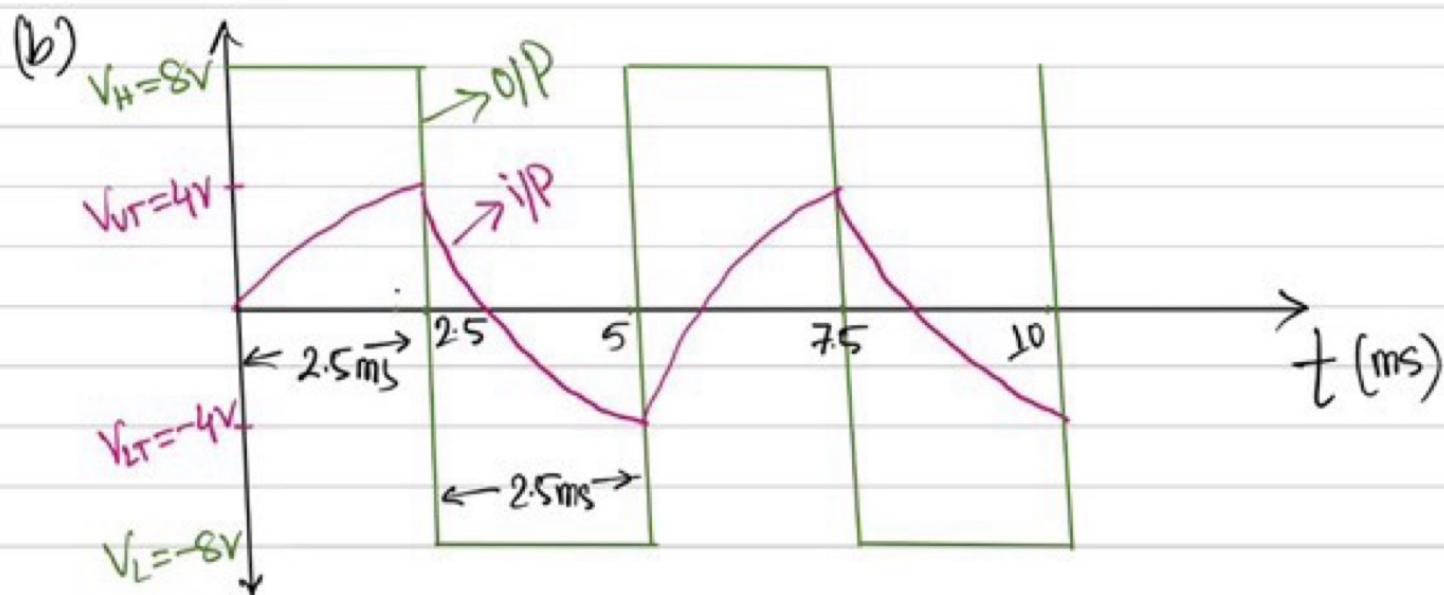$\boxed{R_x = 22.75 K\Omega}$, Time const, $\tau = R_x C_x = 2.27ms$



(c) here $V_L = -V_H$

$V_{UT} = -\frac{R_1}{R_2} V_L = -\frac{V_L}{8} = \frac{V_H}{8}$

$V_{LT} = -\frac{R_1}{R_2} V_H = -\frac{V_H}{8}$

$T_1 = RC \left(\frac{V_{UT} - V_{LT}}{V_H} \right) = RC \left(\frac{\frac{V_H}{8} + \frac{V_H}{8}}{V_H} \right) = \frac{RC}{4}$

$T_2 = RC \left(\frac{V_{LT} - V_{UT}}{V_L} \right) = RC \left(\frac{-\frac{V_H}{8} - \frac{V_H}{8}}{-V_H} \right) = \frac{RC}{4}$

$\therefore T = T_1 + T_2 = \frac{RC}{2}$ $\therefore \boxed{\text{freq, } f = \frac{1}{T} = \frac{2}{RC}}$

Qstn-4 soln ()

(a) Triangular Wave

here $V_L = -V_H$, $p = \frac{40}{10} = 4$

$$\begin{cases} f = \frac{p}{4RC} = \frac{4}{4 \times 2k \times 5\mu f} = 100 \text{ Hz} \\ T = \frac{1}{f} = 10 \text{ ms} \end{cases}$$

(b) From fig-2 $\rightarrow V_H = 8V, V_L = -16V, V_{TH} = 5V, V_{TL} = -10V, T_1 = 0.25 \text{ ms}$

$$V_{TH} = \frac{R_1}{R_1 + R_2} V_H \quad \text{or} \quad V_{TL} = \frac{R_1}{R_1 + R_2} V_L$$

$$5 = \frac{R_1}{R_1 + R_2} \times 8$$

$$-10 = \frac{R_1}{R_1 + R_2} (-16)$$

$$T_1 = R \times C \ln \left| \frac{V_H - V_{TL}}{V_H - V_{TH}} \right|$$

$$0.25 \text{ ms} = R \times 100 \text{ nF} \times 1.79$$

$$R = 1.39 \text{ K}$$

$$\Rightarrow \frac{5}{8} = \frac{R_1}{R_1 + R_2}$$

$$\frac{10}{16} = \frac{R_1}{R_1 + R_2}$$


$$\Rightarrow \frac{5}{3} = \frac{R_1}{R_2}$$

$$R_1 = \frac{5}{3} R_2$$

$$\therefore R_1 = \frac{5}{3} R_2$$

$$\text{Let } R_2 = 30 \text{ K}$$

$$\therefore R_1 = 50 \text{ K}$$

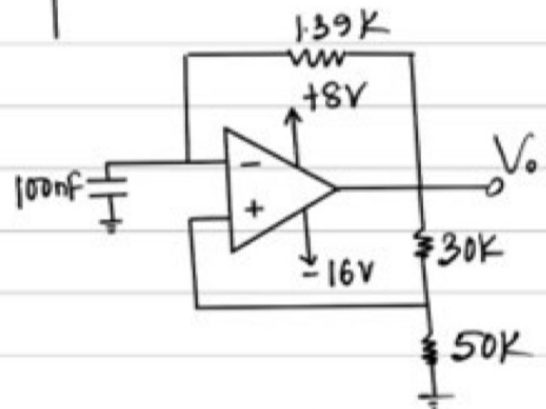

(c) $T_1 = 0.25 \text{ ms}$

$$T_2 = R \times C \ln \left| \frac{V_L - V_{TH}}{V_L - V_{TL}} \right|$$

$$= 1.396 \text{ K} \times 100 \text{ nF} \times \ln \left| \frac{-16 - 5}{-16 + 10} \right|$$

$$T_2 = 0.17 \text{ ms}$$

$$\therefore \text{Period, } T = T_1 + T_2 = 0.42 \text{ ms}$$

$$\text{freq. } f = \frac{1}{T} \approx 2381 \text{ Hz}$$

$$\text{Duty cycle, } D = \frac{T_1}{T} \times 100\%$$

$$= \frac{0.25}{0.42} \times 100\%$$

$$= 59.52\%$$