

Assignment No-01

Name : Tahin Raihan Robbani

Id : 22201344

Course : CSE350

Section : 15

Ans to the Q No-1

(a) Here, $V_{ref} = -10V$, $R_d = 10k\Omega$, $R = 5k\Omega$.

$$I_1 = \frac{V_{ref}}{2R} = \frac{-10}{10} \text{ mA} = -1 \text{ mA}.$$

$$I_2 = \frac{I_1}{2} = \frac{-1}{2} \text{ mA} = -0.5 \text{ mA}.$$

$$I_3 = \frac{I_2}{2} = \frac{-0.5}{2} \text{ mA} = -0.25 \text{ mA}. \quad \underline{\text{Ans}}$$

(b) Resolution or 1 LSB value,

$$V_0 = -V_{ref} \times \frac{R_d}{2R} \left(b_1 + \frac{b_2}{2} + \frac{b_3}{4} \right)$$

$$= -(-10) \times \frac{10}{10} \left(0 + 0 + \frac{1}{4} \right)$$

$$= 2.5 \text{ V}. \quad \underline{\text{Ans}}$$

(c) Maximum value of $V_0 = -V_{ref} \times \frac{R_d}{2R} \left(b_1 + \frac{b_2}{2} + \frac{b_3}{4} \right)$

$$= -(-10) \times \frac{10}{10} \left(1 + \frac{1}{2} + \frac{1}{4} \right)$$

$$= 17.5 \text{ V}.$$

Minimum value of $V_o = -V_{ref} \times \frac{R_2}{2R} (b_1 + \frac{b_2}{2} + \frac{b_3}{4})$
 $= -(-10) \times \frac{19}{10} (0 + 0 + 0)$
 $= 0V.$


Ans

(N) 1 MSB value $= -(-10) \times \frac{19}{10} (1 + 0 + 0) = 10V$

$\therefore \frac{1}{2}$ MSB value $= \frac{10}{2} V = 5V.$

Ans

(e)

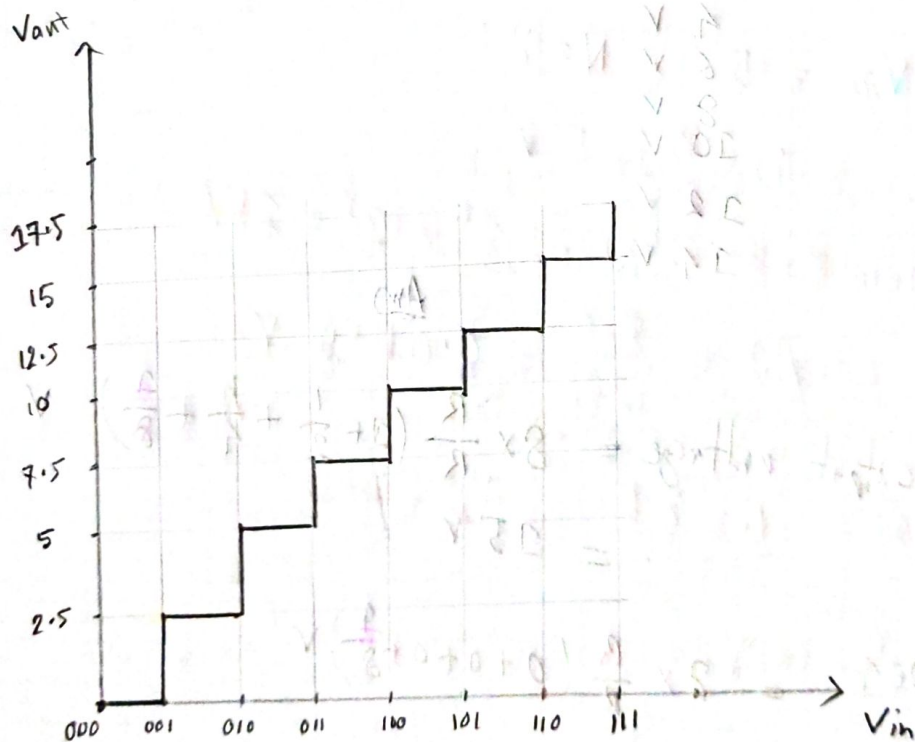

Ans to the Q No-2

(a) $V_e = -8V$, $R_3 = R_f$

So, For XXX0 where X can be 0 or 1,

$$V_o = \cancel{V_{ref}} \times \frac{R_f}{R} \left(b_1 + \frac{b_2}{2} + \frac{b_3}{4} + \frac{b_4}{8} \right)$$

~~where b_1, b_2, b_3, b_4 are the bits of the input~~

$$\therefore V_o = V_{ref} \left(b_1 + \frac{b_2}{2} + \frac{b_3}{4} \right)$$

$$[\because R_f = R \text{ and } b_4 = 0]$$

XXXX	output voltage
0000	0V
0010	2V
0100	4V
0110	6V
1000	8V
1010	10V
1100	12V
1110	14V

Ans

b)

$$\text{Maximum output voltage} = 8 \times \frac{R}{R} \left(1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} \right) V$$

$$= 15V.$$

$$\text{LSB on 0001} = 8 \times \frac{R}{R} \left(0 + 0 + 0 + \frac{1}{8} \right) V$$

$$= 1V.$$

$$\text{Ratio} = \frac{15}{1}$$

ratio of maximum output voltage and LSB is = 15:1.

Ans

(C) Ans $R_3 = R_2$ and it is a BWR DAC,

$$V_o = R_2 \times \left(b_1 \times \frac{V_{ref}}{R_3} + b_2 \times \frac{V_{ref}}{2R_3} + b_3 \times \frac{V_{ref}}{4R_3} + b_4 \times \frac{V_{ref}}{8R_3} \right)$$

$$\Rightarrow V_o = V_{ref} \times \frac{R_2}{R_3} \left(b_1 + \frac{b_2}{2} + \frac{b_3}{4} + \frac{b_4}{8} \right)$$

$$\Rightarrow \frac{R_3}{R_2} = \frac{V_{ref}}{V_o} \left(b_1 + \frac{b_2}{2} + \frac{b_3}{4} + \frac{b_4}{8} \right)$$

$$\Rightarrow \frac{R_3}{R_2} = \frac{8}{5} \left(1 + 0 + \frac{2}{4} + 0 \right) \quad \left[\because V_o = 5V, V_{ref} = 8V \right]$$

and input = 1010

$$\Rightarrow \frac{R_3}{R_2} = 2$$

Ratio of R_3 and R_2 will be = 2:1

Ans to the Q No-3

(a) Here, $V_{ref} = 10V$, $R_1 = 5k\Omega$, $R_2 = 10k\Omega$, $R_3 = 10k\Omega$, $R_4 = 15k\Omega$.

Input in 0-10V,

$$V_1 = 0V$$

$$V_2 = \frac{5}{(5+10+10+15)} (10-0) + 0$$

$$= 1.25V$$

$$V_3 = \frac{15}{40} (10) = 3.75V$$

$$V_4 = \frac{25}{40} \times 10 = 6.25V$$

Quantization Range	Digital output
6.25-10	11
3.75-6.25	10
1.25-3.75	01
0-1.25	00

(b) Using the table from (a) and sample value from table 1

Table from 'a'		Identification of Sample value		
Quantization Range	Digital output	Sampled value	Sampled values quantization range	Sampled values encoded output
6.25-10	11	5	3.75-6.25	10
3.75-6.25	10	7.4	6.25-10	11
1.25-3.75	01	5.71	3.75-6.25	10
0-1.25	00	1.22	0-1.25	00

Ans to the Q No-4

(a) Here $V_{ref} = 5V$, $N = 8 \text{ bit}$.

voltage range is 0 to 5V.

number of steps $= 2^N = 2^8 = 256$

step size of ADC $= \frac{5-0}{256} = 0.0195V$.

Ans

(b) $n = 200$, $N = 8 \text{ bit}$, $V_{ref} = 5V$,

$$V_{input} = \frac{n}{2^N} \times V_{ref}$$

$$= \frac{200}{2^8} \times 5$$

$$= 3.90V$$

Ans

(c) $N = 814$, $n = 200$, $f = 10^6 \text{ Hz}$ so $T = \frac{1}{10^6} \text{ s}$

$$\therefore t_1 = 2^N T = 2^8 \times \frac{1}{10^6} \text{ s} = 2.56 \times 10^{-4} \text{ s}$$

$$\therefore t_2 = nT = 200 \times \frac{1}{10^6} \text{ s} = 2 \times 10^{-4} \text{ s}$$

$$\begin{aligned} \therefore \text{Total reading time} &= (t_1 + t_2) \\ &= (2.56 \times 10^{-4} + 2 \times 10^{-4}) \text{ s} \\ &= 4.56 \times 10^{-4} \text{ s} \end{aligned}$$

(Ans)

(d) max sample rate is when $t_1 = t_2$.

$$\therefore \text{maximum sample rate} = \frac{1}{t_1 + t_2} = \frac{1}{2 \times (2^N T)} = \frac{10^6}{2 \times 2^8} = 1953.12 \text{ Hz}$$

(e) sample rate = $\frac{1}{t_1 + t_2}$

$\therefore$ sample rate $\propto \frac{1}{2^N}$ assuming other ~~parameters~~ ^{parameters} ~~constants~~ ^{constants}.

So if we increase N by 1 sample rate will decrease by 2. So if we wish to increase sample rate by 4 times we have to decrease N by 2 times.

$$\begin{aligned} \therefore \text{counter bits will be} &= (8 - 2) \text{ bit} \\ &= 6 \text{ bit} \end{aligned}$$

Ans