
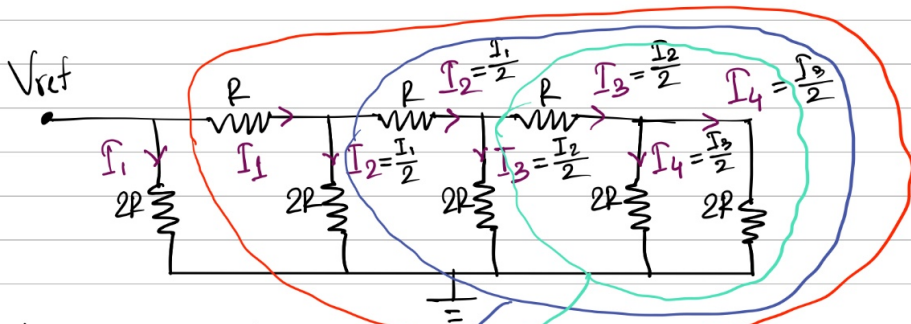


R-2R Ladder DAC

4-bit R-2R DAC

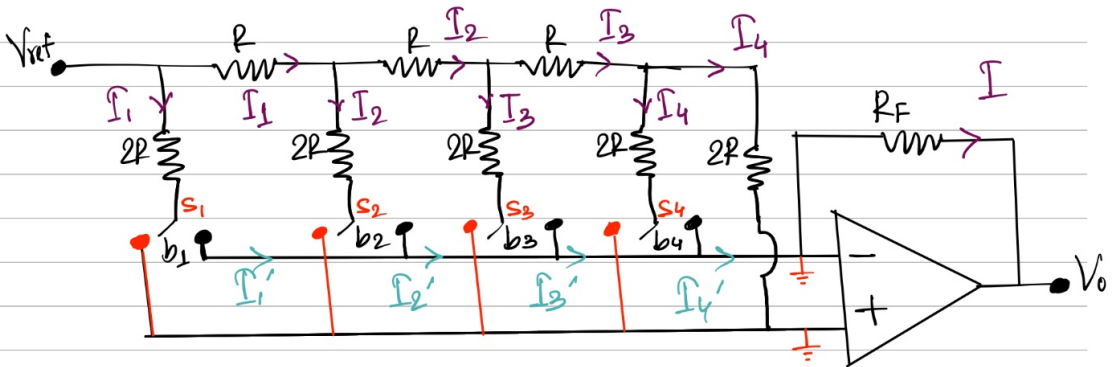

here, $I_1 = \frac{V_{ref} - 0}{2R}$

$$\therefore I_1 = \frac{V_{ref}}{2R}$$

$$\therefore I_2 = \frac{I_1}{2} = \frac{V_{ref}}{4R}$$

$$I_3 = \frac{I_2}{2} = \frac{V_{ref}}{8R}$$

$$I_4 = \frac{I_3}{2} = \frac{V_{ref}}{16R}$$

$$\begin{aligned} & \rightarrow ((2R \parallel 2R) + R) \parallel 2R + R \\ & = (((R + R) \parallel 2R) + R) \parallel 2R + R \\ & = ((2R \parallel 2R) + R) \parallel 2R + R \\ & = (R + R) \parallel 2R + R \\ & = (2R \parallel 2R) + R \\ & = R + R \\ & = 2R \end{aligned}$$

Similarly $\rightarrow 2R$

$\rightarrow 2R$

If $b_1 = 1 \rightarrow S_1$ is connected to inverting i/p $\rightarrow \therefore I'_1 = I_1$

If $b_1 = 0 \rightarrow S_1$ " " " Non-inverting i/p $\rightarrow I'_1 = 0$

$$\therefore I'_1 = b_1 I_1, I'_2 = b_2 I_2, I'_3 = b_3 I_3, I'_4 = b_4 I_4$$

$$\text{here, } I = \frac{0 - V_o}{R_F} = -\frac{V_o}{R_F}$$

Applying KCL

$$I = I_1' + I_2' + I_3' + I_4'$$

$$\Rightarrow -\frac{V_o}{R_F} = b_1 I_1 + b_2 I_2 + b_3 I_3 + b_4 I_4$$

$$\Rightarrow -\frac{V_o}{R_F} = b_1 \frac{V_{ref}}{2R} + b_2 \frac{V_{ref}}{4R} + b_3 \frac{V_{ref}}{8R} + b_4 \frac{V_{ref}}{16R}$$

$$\Rightarrow V_o = -V_{ref} \frac{R_F}{2R} \left(b_1 + \frac{b_2}{2} + \frac{b_3}{4} + \frac{b_4}{8} \right)$$

let 4 bit


* Step size $\rightarrow$ 1 LSB value $\rightarrow V_o$ corresponds to 0001

* 1 MSB value $\rightarrow V_o$ corresponds to 1000

* Max o/p voltage $\rightarrow V_o$ " " 1111 $\rightarrow V_{max}$

* Min o/p " $\rightarrow V_o$ " " 0000 $\rightarrow V_{min}$

Practice Problem

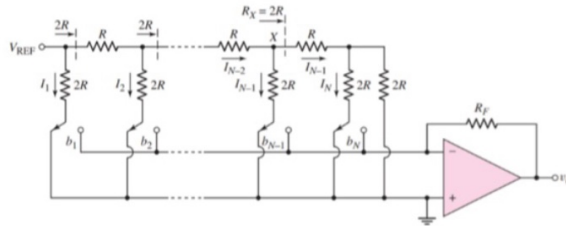

The N -bit D/A converter with an R - $2R$ ladder network in the above figure is to be designed as a 6-bit D/A device. Suppose $V_{REF} = -5V$ and $R_F = R = 5k\Omega$.

(a)	Find currents $I_1, I_2, I_3, I_4, I_5, I_6$.
(b)	What is the output voltage if the input is 010011?
(c)	What is the change in output voltage if the input changes from 101010 to 010101?

$$a) I_1 = \frac{V_{REF}}{2R} = \frac{-5}{10} \Rightarrow I_1 = -0.50mA$$

$$I_2 = \frac{I_1}{2} = -0.25mA$$

$$I_3 = \frac{I_2}{2} = -0.125mA$$

$$I_4 = \frac{I_3}{2} = -0.0625mA$$

$$I_5 = \frac{I_4}{2} = -0.03125mA$$

$$I_6 = \frac{I_5}{2} = -0.015625mA$$

$$b) \text{ Input} = 010011$$

$$V_o = -[I_2 + I_5 + I_6] R_F = [0.25 + 0.03125 + 0.015625]mA \times 5k\Omega = 1.484375V$$

$$c) \text{ Input} = 101010$$

$$V_o = -[I_1 + I_3 + I_5] R_F = [0.50 + 0.125 + 0.03125]mA \times 5k\Omega = 3.28125V$$

$$\text{Input} = 010101$$

$$V_o = -[I_2 + I_4 + I_6] R_F = [0.25 + 0.0625 + 0.015625]mA \times 5k\Omega = 1.640625V$$

$$\Delta V_o = 1.640625V$$