

Solve


ID:	Name:
-----	-------

Brac University
Semester: Spring 2025
Course Code: CSE250
Circuits and Electronics
Section: 07

Assessment: Assignment 3
Full Marks: 20

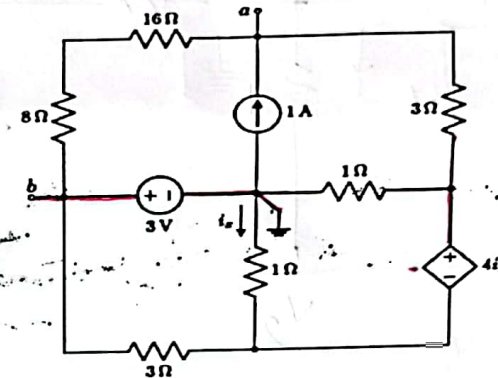Question 1 of 2

Consider the following circuit with terminal a and b. Currently no load is connected to the terminals.




- Draw the equivalent circuit using Thevenin theorem.
- Find the Norton equivalent current.

[2] 6
[2] 4

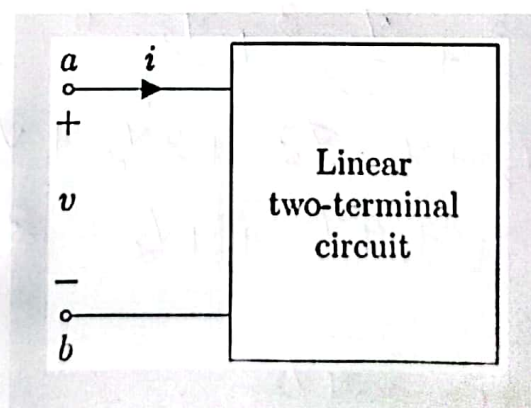Question 2 of 2:


Following is the unknown circuit. Except the two terminal other part of the circuit is not accessible. After applying 30 V to the terminal, 1 A current was measured with terminal a-b. Similarly, after applying 50 V, 3 A current was measured.



- Find the I-V equation of the unknown circuit.
- From the equation derive the equivalent circuit (Either in Voltage Source- Resistance form or Current Source-Resistance form).

[3] 6
[2] 4

1. For, V_{Th}

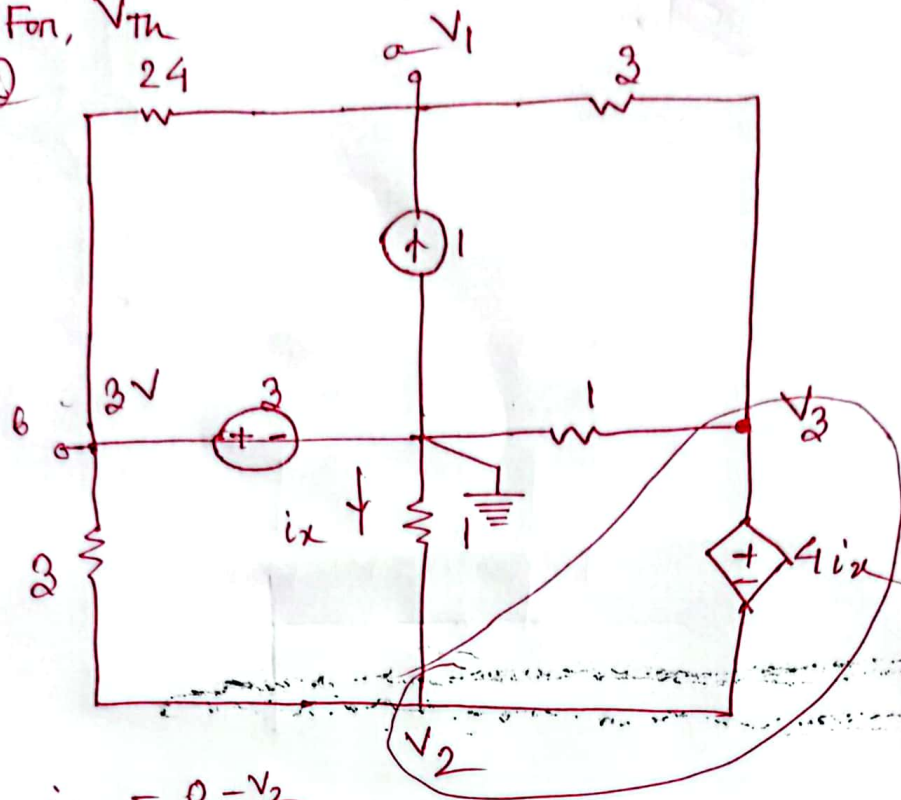

$$i_x = \frac{0 - V_2}{1}$$

$$i_x = -V_2$$

At node, ①, $\frac{V_1 - 3}{24} + \frac{V_1 - V_3}{3} - 1 = 0$

$$V_1 - 3 + 8V_1 - 8V_3 - 24 = 0$$

$$\Rightarrow 9V_1 - 8V_3 = 27 \quad \text{--- (I)}$$

at supernode, ② & ③,

$$\frac{V_2 - 0}{1} + \frac{V_2 - 3}{3} + \frac{V_3 - 0}{1} + \frac{V_3 - V_1}{3} = 0$$

$$\Rightarrow 3V_2 + V_2 - 3 + 3V_3 + V_3 - V_1 = 0$$

$$\Rightarrow -V_1 + 4V_2 + 4V_3 = 3 \quad \text{--- (II)}$$

$$V_3 - V_2 = 4i_x$$

$$\Rightarrow V_3 - V_2 = -4V_2$$

$$\Rightarrow V_3 + 3V_2 = 0$$

$$\Rightarrow 3V_2 + V_3 = 0 \quad \text{--- (III)}$$


$$V_1 = 6V$$

$$V_2 = -1.125V$$

$$V_3 = 2.375V$$

$$V_{Th} = V_{ab} = V_a - V_b = 6 - 3 = 3V$$

For R_{th}

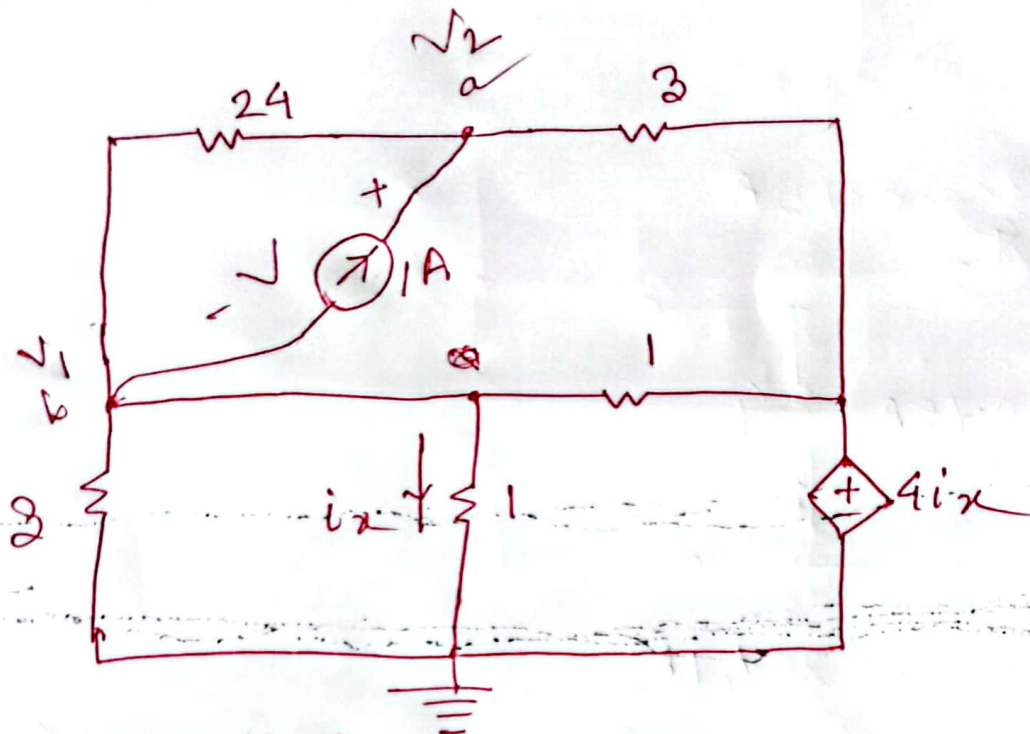

$$i_x = \frac{v_1 - 0}{1} = v_1$$

at node ①,

$$\frac{v_1}{3} + 1 + \frac{v_1 - v_2}{24} + \frac{v_1}{1} + \frac{v_1 - 4i_x}{1} = 0$$

$$\Rightarrow \frac{v_1}{3} + 1 + \frac{v_1 - v_2}{24} + v_1 - 4v_1 = 0$$

$$\Rightarrow 8v_1 + 24 + v_1 - v_2 - 48v_1 = 0$$

$$\Rightarrow -39v_1 - v_2 = -24 \quad \text{--- (i)}$$

at node ②,


$$-1 + \frac{v_2 - v_1}{24} + \frac{v_2 - 4i_x}{3} = 0$$

$$\Rightarrow -1 + \frac{v_2 - v_1}{24} + \frac{v_2 - 4v_1}{3} = 0$$


$$\Rightarrow -24 + v_2 - v_1 + 8v_2 - 32v_1 = 0$$

$$\Rightarrow -33v_1 + 9v_2 = 24 \quad \text{--- (ii)}$$
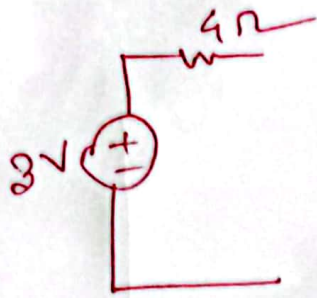
$$v = v_2 - v_1 = 4V, \quad R_{th} = \frac{v}{1} = \frac{4}{1} \Omega = 4\Omega$$


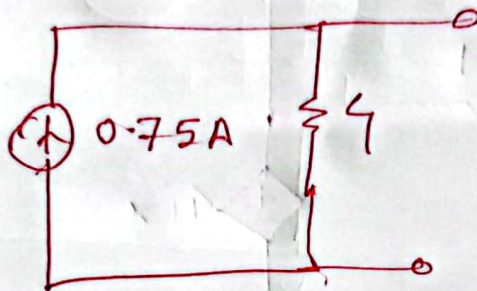
$$b) \quad I_N = \frac{3}{4} = 0.75 \text{ A}$$



2. (a) First point: (30V, 1A)

Second point: (50V, 3A)

$$\begin{aligned} \frac{I - 1}{1 - 3} &= \frac{V - 30}{30 - 50} \left[\frac{x - x_1}{x_1 - x_2} = \frac{y - y_1}{y_1 - y_2} \right] \\ \Rightarrow \frac{I - 1}{-2} &= \frac{V - 30}{-20} \\ \Rightarrow I - 1 &= \frac{V - 30}{10} \\ \Rightarrow I &= \frac{V}{10} - 2 \end{aligned}$$

(b)



$$I = \frac{V}{R} - \frac{V_s}{R}$$

$$\frac{1}{R} = \frac{1}{10}$$

$$R = 10 \Omega,$$

$$\frac{V_s}{R} = 2$$
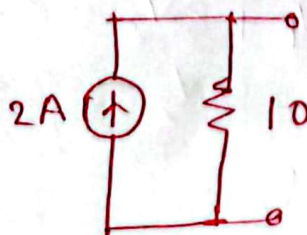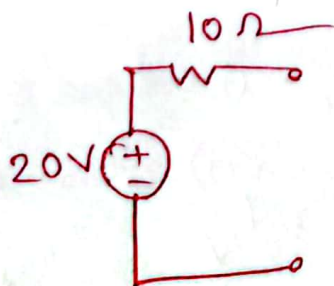
$$\frac{V_s}{10} = 2 \Rightarrow V_s = 20 \text{ V}$$



$$I_s = \frac{V_s}{R} = \frac{20}{10} = 2$$