

CSE 460: VLSI Design

Lecture 9: Finite State Machines (part 2)

Example 2: A Simple Input Pattern ('11' Overlapping Sequence) Detection Circuit (Mealy Type)


Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	1	0	0	1	1	0	0

Figure 6.22 Sequences of input and output signals.

Steps->

- State diagram
- State table
- State assigned table
- K-map
- Circuit

 Example 2: A Simple Input Pattern ('11' Overlapping Sequence) Detection Circuit (Mealy Type)



Steps->

- **State diagram**
- State table
- State assigned table
- K-map
- Circuit

Figure 6.23 State diagram of an FSM that realizes the task in Figure 6.22.

Example 2: A Simple Input Pattern ('11' Overlapping Sequence) Detection Circuit (Mealy Type)

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

Figure 6.24 State table for the FSM in Figure 6.23.

Steps->

- State diagram
- **State table**
- **State assigned table**
- K-map
- Circuit

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

Figure 6.25 State-assigned table for the FSM in Figure 6.24.

Note that,

➤ $Y = f(w, y)$

➤ $z = f(w, y)$

Example 2: A Simple Input Pattern ('11' Overlapping Sequence) Detection Circuit (Mealy Type)

Y =>

y \ w	0	1
0	0	1
1	0	1

$$Y = w$$

z =>

y \ w	0	1
0	0	0
1	0	1

$$z = wy$$


Steps->

- State diagram
- State table
- State assigned table
- **K-map** (Y and z)
- Circuit

Note that,

- $Y = f(w, y)$
- $z = f(w, y)$

 Example 2: A Simple Input Pattern ('11' Overlapping Sequence) Detection Circuit (Mealy Type)




Steps->

- State diagram
- State table
- State assigned table
- K-map
- **Circuit**

Mealy Type FSM

 ⊕ Detecting Sequence: "101" (Overlapping)



Present state (y _{2y₁})	Next state (y _{2y₁})		Output (z)	
	w=0	w=1	w=0	w=1
(00) A	A(00)	B(01)	0	0
(01) B	C(10)	B(01)	0	0
(10) C	A(00)	B(01)	0	1


∴ No of Flip-Flop = No of bits in Present state
= 3

Example 3: A Simple Input Pattern ('101' Overlapping Sequence) Detection Circuit (Mealy Type)

Important:

In Mealy Type FSM, you do not need to declare a separate state for your final output (for this example: no separate state for '101' is required). After getting your output $z = 1$, you will start your 2nd loop (Start finding $z=1$ for the 2nd time).

 Detecting Sequence "101" (Non-overlapping)



Present state ($y_2 y_1$)	Next state ($y_2 y_1$)		Output (z)	
	w=0	w=1	w=0	w=1
(00) A	A(00)	B(01)	0	0
(01) B	C(10)	B(01)	0	0
(10) C	A(00)	A(00)	0	1

**Example 4: A Simple Input Pattern
(‘101’ Non-Overlapping Sequence)
Detection Circuit (Mealy Type)**

Example 5:

1.	1. A finite state machine that has to generate $z = 1$ when the previous four values of input w were 1001 or 1111; otherwise, $z = 0$. Overlapping input patterns are allowed. The machine also has a negative reset. An example of the desired behavior is		
	w : 0101 1110 0110 0111 11 z : 0000 0010 0100 0100 11		
	(a)	Design the state diagram. Mark your reset states and transitions clearly. Is this machine Mealy type or Moore type?	3
	(b)	Derive the assigned table and write the Verilog code to implement the following FSM.	4
	(c)	Validate your answer with the appropriate input and output waveforms on a timing diagram. Include all possible combinations of the input (w).	3

Solution:


The Machine is Mealy type

My Reset state is A State

W = Input Sequence

Z = Output

Format is W/Z

 

Present State	Next State		Output	
	W=0	W=1	W=0	W=1
A	A	B	0	0
B	C	E	0	0
C	D	B	0	0
D	A	B	0	1
E	C	F	0	0
F	C	F	0	1

State Assigned Table:

A = 000
 B = 010
 C = 011
 D = 011
 E = 100
 F = 101


Present state	Next State		Out put	
	W=0	W=1	W=0	W=1
000	000	001	0	0
001	010	100	0	0
010	011	001	0	0
011	000	001	0	1
100	010	101	0	0
101	010	101	0	1

Example 6:

The input-output behavior of a sequence detector FSM is given below.																			
<i>CLK</i>	<i>t</i> ₁	<i>t</i> ₂	<i>t</i> ₃	<i>t</i> ₄	<i>t</i> ₅	<i>t</i> ₆	<i>t</i> ₇	<i>t</i> ₈	<i>t</i> ₉	<i>t</i> ₁₀	<i>t</i> ₁₁	<i>t</i> ₁₂	<i>t</i> ₁₃	<i>t</i> ₁₄	<i>t</i> ₁₅	<i>t</i> ₁₆	<i>t</i> ₁₇	<i>t</i> ₁₈	
<i>w</i>	1	0	0	1	1	1	0	0	0	0	0	0	0	0	1	0	0	0	
<i>z</i>	0	1	0	1	0	0	1	0	0	0	0	0	0	0	1	1	0	0	
(a)	Identify the <u>sequence</u> and the <u>type</u> of FSM for the above input-output combinations. [<u>Hint</u> : The above table contains two sequences]																		1+1
(b)	Design the state diagram, the state table, and the <i>gray-encoded</i> state assigned table. [Overlapping allowed].																		3+2+ 2
(c)	Determine the logic expressions of the next state and output variables using k-maps.																		6

- ** Alternating 0 and 1
- ** Two consecutive inputs are different

Solution:

 

Present State	Next State		Output z	
	$w=0$	$w=1$	$w=0$	$w=1$
A	B	A C	0	0
B	B	A C	0	1
C	B	C	1	0

Present state	Next State		Output z	
	$w=0$	$w=1$	$w=0$	$w=1$
00	01	10	0	0
01	01	10	0	1
10	01	10	1	0


Example: 07: Double input FSM

Consider a sequential circuit with two inputs ($u1$ & $u2$) and a single output, z . CLEO is a prestigious conference where researchers from all over the world submit their research articles. These articles are handled by an **Editor** and a **Reviewer**. They review each article *independently*, and either approve a submitted article (denoted by 1) or reject it (denoted by 0). The decisions of the **Editor** are given by a bit stream, $u1$, whereas the decisions of the **Reviewer** are given by $u2$. If for three consecutive articles, both of their decisions are the same (i.e. $u1 = u2$ for three consecutive clock cycles), then they receive a consistency reward ($z = 1$) from the conference committee after a period.

Here, the decisions of the Editor & the Reviewer for a number of submitted articles & their corresponding reward instances are given below:

$u1$	0	1	1	0	1	1	1	0	0	0	1
$u2$	1	1	1	0	0	0	1	0	0	1	1
z	0	0	0	0	1	0	0	0	0	1	0

(a)	What type of FSM would you need for the given problem?	1
(b)	Design the state diagram for the corresponding FSM.	4
(c)	Derive the state-assigned table from your state diagram in (a).	4
(d)	Evaluate the <u>next state</u> & <u>output</u> logic expressions to implement the FSM & calculate the number of flip-flops required for the circuit implementation. (You don't need to draw the circuit implementation.)	5 + 1

 

Example: 07: Double output FSM

CLK	1	2	3	4	5	6	7	8	9	10	11	12	13
w	0	1	0	1	0	0	0	0	1	1	0	0	1
Z1	0	0	1	1	1	1	0	0	0	1	0	1	0
Z2	0	0	0	0	0	0	1	1	1	0	1	0	1


Solution: Moore Type FSM

For,

$w = 01$ or 10 , $Z1 = 1$ and $Z2 = 0$

For,

$w = 00$ or 11 , $Z1 = 0$ and $Z2 = 1$

 

Present State (Y ₂ Y ₁ Y ₀)	Next State (M ₂ M ₁ M ₀)		Output	
	W = 0	W = 1	Z ₂	Z ₁
A(000)	B	D	0	0
B(001)	C	F	0	0
C(010)	C	F	1	0
D(011)	E	G	0	0
E(100)	C	F	0	1
F(101)	E	G	0	1
G(110)	E	G	1	0
H(111)	d	d	d	d

Example: 08: Double output FSM

CLK	1	2	3	4	5	6	7	8	9	10	11	12	13
w	0	1	0	1	0	0	0	0	1	1	0	0	1
Z1	0	0	1	0	1	0	0	0	0	1	0	0	0
Z2	0	0	0	0	0	0	1	1	1	0	0	0	1


Solution: Moore Type FSM

For,

$w = 01$, $Z1 = 1$ and $Z2 = 0$

For,

$w = 00$, $Z1 = 0$ and $Z2 = 1$

 

Example: 09: Double output FSM

CLK	1	2	3	4	5	6	7	8	9	10	11	12	13
w	0	1	0	1	0	0	0	0	1	1	0	0	1
Z1	0	0	1	0	1	0	0	0	0	1	0	0	0
Z2	0	0	0	1	0	1	0	0	0	0	0	1	0


Solution: Moore Type FSM

For,

w = 01, Z1 = 1 and Z2 = 0

For,

w = 10, Z1 = 0 and Z2 = 1

 

Encoding Schemes (State Assignment)

Consider a state assigned table below:

	Present state	Next state		Output <i>z</i>
		<i>w=0</i>	<i>w=1</i>	
	<i>y₂ y₁</i>	<i>Y₂ Y₁</i>	<i>Y₂ Y₁</i>	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	<i>dd</i>	<i>dd</i>	<i>d</i>

Schemes->

- Binary encoding
- Gray encoding
- One-hot encoding

Encoding Schemes (State Assignment)

Consider another state assigned table below:

	Present state	Next state		Output <i>z</i>
		<i>w=0</i>	<i>w=1</i>	
	<i>y₂ y₁</i>	<i>Y₂ Y₁</i>	<i>Y₂ Y₁</i>	
A	00	00	01	0
B	01	00	11	0
C	11	00	11	1
	10	<i>dd</i>	<i>dd</i>	<i>d</i>

Schemes->

- Binary encoding
- **Gray encoding**
- One-hot encoding

Decimal Number	4 bit Binary Number	4 bit Gray Code
	<u>ABCD</u>	<u>G₁G₂G₃G₄</u>
0	0 0 0 0	0 0 0 0
1	0 0 0 1	0 0 0 1
2	0 0 1 0	0 0 1 1
3	0 0 1 1	0 0 1 0
4	0 1 0 0	0 1 1 0
5	0 1 0 1	0 1 1 1
6	0 1 1 0	0 1 0 1
7	0 1 1 1	0 1 0 0
8	1 0 0 0	1 1 0 0
9	1 0 0 1	1 1 0 1
10	1 0 1 0	1 1 1 1
11	1 0 1 1	1 1 1 0
12	1 1 0 0	1 0 1 0
13	1 1 0 1	1 0 1 1
14	1 1 1 0	1 0 0 1
15	1 1 1 1	1 0 0 0

Encoding Schemes (State Assignment)

Consider another state assigned table below:

	Present state $y_3y_2y_1$	Next state		Output z
		$w = 0$	$w = 1$	
		$Y_3Y_2Y_1$	$Y_3Y_2Y_1$	
A	0 0 1	0 0 1	0 1 0	0
B	0 1 0	0 0 1	1 0 0	0
C	1 0 0	0 0 1	1 0 0	1

Schemes->

- Binary encoding
- Gray encoding
- **One-hot encoding**

How many flipflops are required? **Ans: 3**