

Semester: **Spring 2023**
Course Code: **CSE460**
Course Title: **VLSI Design**


Midterm Exam
Full Marks: **15 x 3 = 45**
Time: **1 hour 30 minutes**
Date: **4th March 2023**

Set A

Student ID:	Name:	Section:
-------------	-------	----------

[Answer any **THREE** questions out of **FOUR**. Each question carries equal marks.]

[After the exam, the question paper should be turned in along with the answer script.]

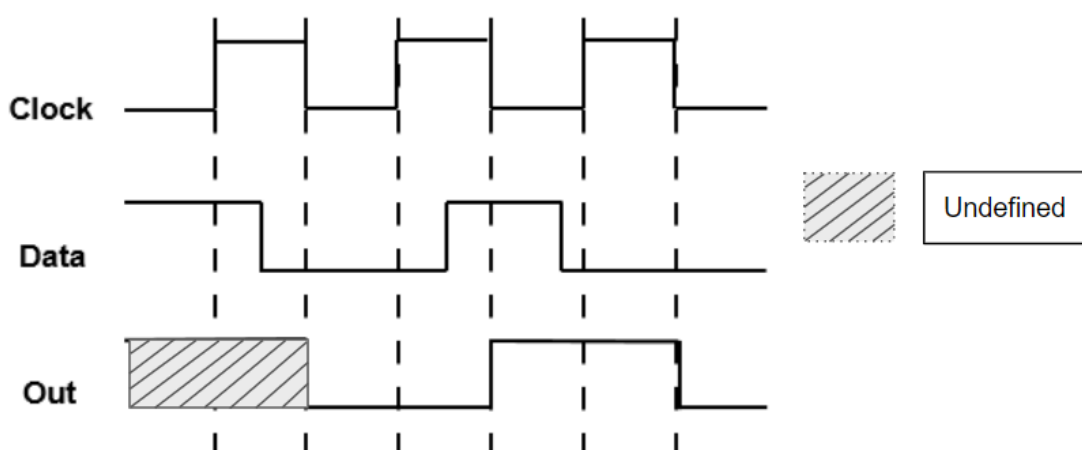1. (CO1)	The timing diagram of an edge triggered sequential circuit element is shown in Figure 1		
	 Figure 1		
	(a)	Identify the type of the edge triggered circuit element shown in Figure 1 .	3
	(b)	Justify if it is possible to build the circuit element as shown in Figure 1 using level triggered sequential circuit elements only. Draw the appropriate block diagrams.	6
	(c)	Draw the appropriate circuit diagrams corresponding to the block diagrams of (b) using transmission gates.	6

2. (CO3)	Observe Figure 2 and answer the following questions. Figure 2: Top view of a wafer after fabricating an n+ diffusion region (dark region) <table border="1" data-bbox="323 667 1374 846"> <tr> <td data-bbox="323 667 395 748">(a)</td><td data-bbox="395 667 1374 748">Draw the cross-sectional view of the above figure along ‘Line A’ and label the different regions.</td><td data-bbox="1374 667 1449 748">3</td></tr> <tr> <td data-bbox="323 748 395 846">(b)</td><td data-bbox="395 748 1374 846">Briefly describe and illustrate the necessary steps to fabricate the n+ diffusion region on a blank wafer as shown in the figure.</td><td data-bbox="1374 748 1449 846">12</td></tr> </table>	(a)	Draw the cross-sectional view of the above figure along ‘Line A’ and label the different regions.	3	(b)	Briefly describe and illustrate the necessary steps to fabricate the n+ diffusion region on a blank wafer as shown in the figure.	12				
(a)	Draw the cross-sectional view of the above figure along ‘Line A’ and label the different regions.	3									
(b)	Briefly describe and illustrate the necessary steps to fabricate the n+ diffusion region on a blank wafer as shown in the figure.	12									
3. (CO3)	Figure 3 Figure 4 <table border="1" data-bbox="323 1433 1374 1653"> <tr> <td data-bbox="323 1433 395 1514">(a)</td><td data-bbox="395 1433 1374 1514">i) Design the CMOS compound gate for output Y from the given stick diagram in Figure 3. Clearly indicate the PUN and PDN networks.</td><td data-bbox="1374 1433 1449 1514">4+4</td></tr> <tr> <td data-bbox="323 1514 395 1572"></td><td data-bbox="395 1514 1374 1572">ii) Find the layout area of Figure 3 in terms of Lambda (λ).</td><td data-bbox="1374 1514 1449 1572">1</td></tr> <tr> <td data-bbox="323 1572 395 1653">(b)</td><td data-bbox="395 1572 1374 1653">Identify the connection errors in the stick diagram for the compound gate, $Y = AB + \bar{C}$ in Figure 4. Design the correct stick diagram for Y.</td><td data-bbox="1374 1572 1449 1653">6</td></tr> </table>	(a)	i) Design the CMOS compound gate for output Y from the given stick diagram in Figure 3 . Clearly indicate the PUN and PDN networks.	4+4		ii) Find the layout area of Figure 3 in terms of Lambda (λ).	1	(b)	Identify the connection errors in the stick diagram for the compound gate, $Y = AB + \bar{C}$ in Figure 4 . Design the correct stick diagram for Y.	6	
(a)	i) Design the CMOS compound gate for output Y from the given stick diagram in Figure 3 . Clearly indicate the PUN and PDN networks.	4+4									
	ii) Find the layout area of Figure 3 in terms of Lambda (λ).	1									
(b)	Identify the connection errors in the stick diagram for the compound gate, $Y = AB + \bar{C}$ in Figure 4 . Design the correct stick diagram for Y.	6									

4. (CO2)	You are tasked with designing a CD/DVD drive's control circuitry using a <i>Moore</i>-type finite-state machine. The drive has one input push button w, which generates $w = 1$ when pushed, and $w = 0$ when un-pushed. A $w = 1$ input causes the tray to open if it was already closed, or causes the tray to close if it was already open. The control circuit has only one output signal, z, which determines if the CD/DVD drive should be open ($z = 1$) or closed ($z = 0$) with the following instructions: • If the tray is closed, pushing the button (setting $w = 1$) should generate the signal ($z = 1$) to open the tray • If the tray has been open for less than 3 clock cycles, pushing the button (setting $w = 1$) should generate the signal ($z = 0$) to close the tray • The tray should automatically close after being open for 3 clock cycles • For simplicity, assume that the time required for opening and closing the tray is negligible compared to the system clock's time period 	
(a)	Determine the frequency of the system clock if the tray won't stay open for more than 5 seconds.	2
(b)	Draw the state diagram for the machine.	5
(c)	Derive a state-assigned table from (b) using the <i>gray</i> -encoding technique.	3
(c)	Find the next-state and output logic expressions using k-map.	5